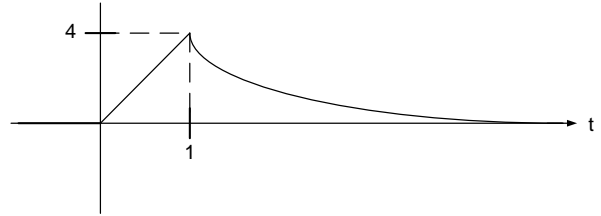



1. **Given** $v(t) = \begin{cases} 0, & t \leq 0, \\ 4t, & 0 < t \leq 1 \\ 4e^{-(t-1)}, & t > 1 \end{cases}$

across a $\frac{1}{2} \mu F$ capacitor



- Find** $i(t)$ through it
- Find** $p(t)$ delivered to it (power)
- Find** $w(t)$ stored in it (energy)
- Find** $\int_0^\infty p(t) dt$ and comment on its significance

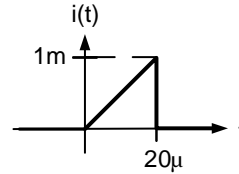2. **Given** $i(t) = \begin{cases} 0, & t \leq 0 \text{ s}, \\ 500t, & 0 < t \leq 20 \mu s \\ 0, & t > 20 \mu s \end{cases}$



is delivered to an uncharged $0.2 \mu F$ cap.

- Find** $v(t)$ across the capacitor for $t \geq 0$
- Why does a voltage remain on the capacitor after the current is zero from an intuitive viewpoint?

3. **Given** the following circuit

Find v_1 , v_2 , v_3 , i_1

