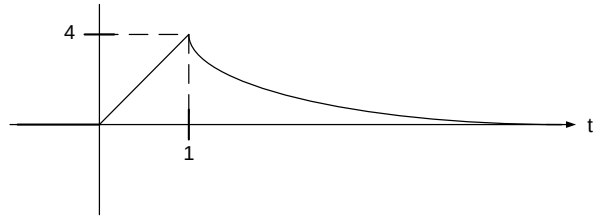


1. Given $v(t) = \begin{cases} 0, & t \leq 0, \\ 4t, & 0 < t \leq 1 \\ 4e^{-(t-1)}, & t > 1 \end{cases}$

across a $\frac{1}{2} \mu F$ capacitor



- Find** $i(t)$ through it
- Find** $p(t)$ delivered to it (power)
- Find** $w(t)$ stored in it (energy)
- Find** $\int_0^\infty p(t) dt$ and comment on its significance

a) $i = C v'$

$$= \begin{cases} 0 A, & t \leq 0 \\ (0.5 \mu)(4) = 2 \mu A, & 0 < t \leq 1 \\ (0.5 \mu)(-4e^{-(t-1)}) = -2e^{-(t-1)} \mu A, & t > 1 \end{cases}$$

b) $p = i \cdot v$

$$= \begin{cases} 0 W, & t \leq 0 \\ (4t)(2 \mu) = 8t \mu W, & 0 < t \leq 1 \\ 4e^{-(t-1)}(-2e^{-(t-1)} \mu) = -8e^{-2(t-1)} \mu W, & t > 1 \end{cases}$$

c) $w = \frac{1}{2} C v^2$

$$= \begin{cases} 0 J, & t \leq 0 \\ \frac{1}{2} \frac{1}{2} \mu (4t)^2 = 4t^2 \mu J, & 0 < t \leq 1 \\ \frac{1}{2} \frac{1}{2} \mu (16e^{-2(t-1)}) = 4e^{-2(t-1)} \mu J, & t > 1 \end{cases}$$

d) Painful way: $\int_0^\infty p(t) dt = \int_0^1 p(t) dt + \int_1^\infty p(t) dt$


and substitute in values of $p(t)$ found in part (b). Ouch.

Smart way: $\int_0^\infty p(t) dt = w(\infty) - w(0)$ (integral of power is work)

$$= 4e^{-2\infty} - 0$$

$$= \boxed{0} \text{ much easier!}$$

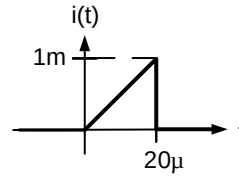2. Given $i(t) = \begin{cases} 0, & t \leq 0, \\ 500t, & 0 < t \leq 20\mu s \\ 0, & t > 20\mu s \end{cases}$



is delivered to an uncharged $0.2\mu F$ cap.


- Find $v(t)$ across the capacitor for $t \geq 0$.
- Why does a voltage remain on the capacitor after the current is zero from an intuitive viewpoint?

a) Region	t_0	$i(t)$	$v(t_0)$	$v(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$
$t < 0$	$-\infty$	0	0	$= \frac{1}{C} \int_{-\infty}^t 0 d\tau + 0 = 0$
$0 < t < 20\mu$	0	$500t$	0	$= (5M) \int_0^t 500\tau d\tau + 0 = (5M)(250t^2) = 12.5t^2 V$
$t > 20\mu$	20μ	0	$12.5(20\mu)^2 V$ $= 12.5(400p) V$ $= 5$	$= 0 + 5 = 5V$


b) After $20\mu s$, $5V$ of "pressure" is stored in the stretched elastic "diaphragm". With the current set to zero, no further movement of the diaphragm is possible. & the voltage remains $5V$.

3. Given the following circuit

Find v_1 , v_2 , v_3 , i_1

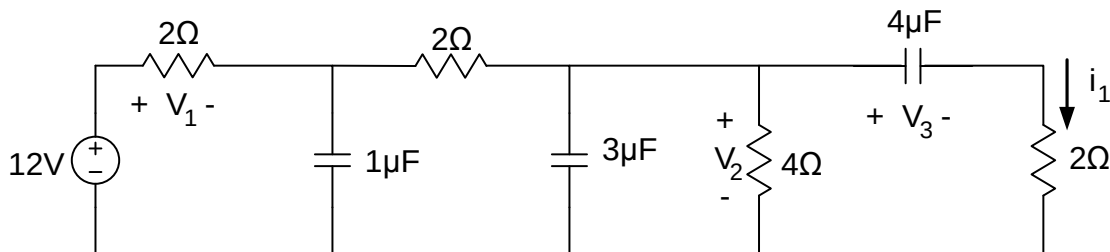

DC steady-state, so caps look like opens

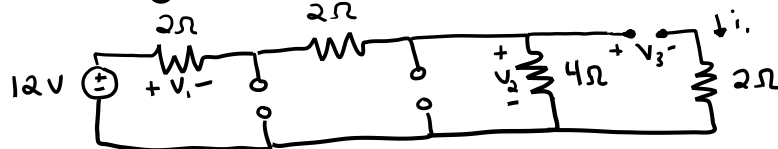

By voltage divider, $V_1 = \frac{2}{2+2+4} 12 = \boxed{3V}$, $V_2 = \frac{4}{2+2+4} 12 = \boxed{6V}$

$i_1 = 0A$, and KVL around right loop: $-V_2 + V_3 + i_1 \cdot 2 = 0 \Rightarrow \boxed{V_3 = 6V}$