

1. Find  $C_{eq}$  if all capacitors are  $1\mu\text{F}$ .

