


# Capacitor

- Tries to keep voltage constant

$$Q = C \cdot V$$

$$i = C \cdot v'$$


Ex

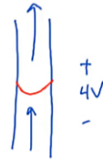

battery: 12V supply max 500A  
but big bass thump (10ms) draws 1000A  
what happens 12V can't supply, V drops, ☹️

Soln Capacitor

Intuition

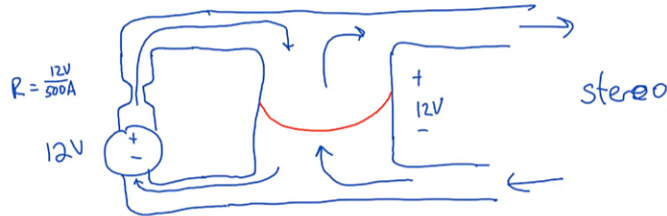

Math  $Q = \int i(t) dt = (1000A)(10ms) = 10C$

$$Q = C \cdot V = (5)(12) = 60C$$

$$\begin{aligned} \Delta V_c &= \frac{1}{C} \int_{t_0}^{t_1} i_c(\tau) d\tau \\ &= \frac{1}{5} \int_0^{10m} 500 d\tau \\ &= 100 \int_0^{10m} d\tau \\ &= 100 \tau \Big|_{\tau=0}^{10m} \\ &= 1000m - 0 \\ &= 1V \end{aligned}$$