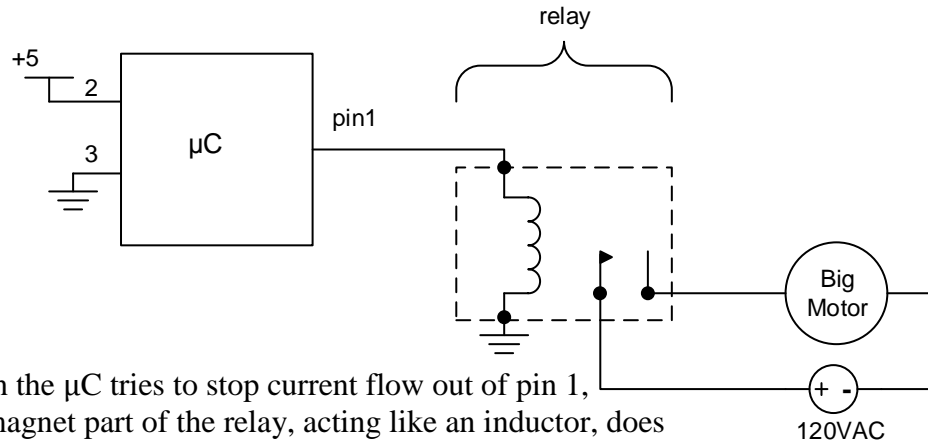


1. A relay is a momentary switch activated by an electromagnet (i.e., an inductor) allowing a small current low voltage source (like a microcontroller) to control heavy-duty sources (like an AC muter). In the circuit below, a microcontroller (abbrev.  $\mu C$ ) turns on a relay by making pin 1 = 5V at  $t=0$  sec. At  $t=1$  sec it turns the relay off by trying to stop current flow out of pin 1 (internally disconnecting it).



At  $t=1$  when the  $\mu C$  tries to stop current flow out of pin 1, the electromagnet part of the relay, acting like an inductor, does

- Nothing
- Tries to make the voltage at pin large and positive
- Tries to make the voltage at pin large and negative
- Tries to make the voltage at pin large and equal to zero

By math


$V = L \frac{di}{dt}$  so if  $i'$  is very large and negative then  $V$  is large and negative.

By intuition

The inductor wants to keep current flowing down so it must create a voltage to try to pull it out of the  $\mu C$ . To "pull it out" it goes large and negative.

2. Could the action described in the preceding paragraph damage the  $\mu C$ ? If so, how could you use a diode to help? A diode,  $\rightarrow|$ , is a device that only allows current to flow in the direction of the arrow (i.e. it looks like a short to current flowing in the direction of the arrow, but an open current flowing in reverse).

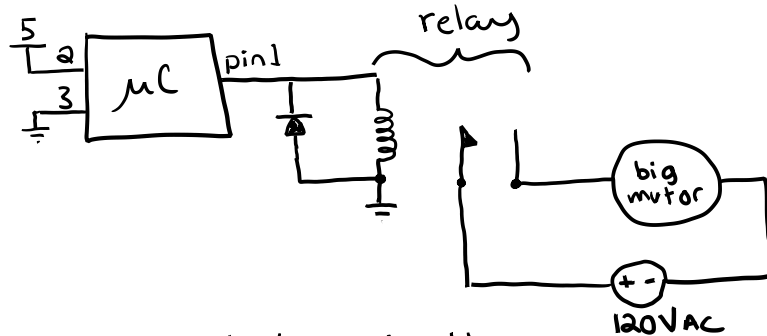Yes it could damage the  $\mu C$ ; the voltage could be huge (perhaps > several hundred volts).  
To fix this, try this:



Normally the diode looks like an open, until pin suddenly turns off. Then  $V_{pin} < 0$  and the diode becomes an open, keeping  $V_{pin}$  from going much less than 0.

Note: In reality, most relays require about 100mA of current to work, but  $\mu C$  can only supply about 10mA so an additional current amplifier is needed. That is typically a FET, a type of transistor you'll meet in EE 355.