
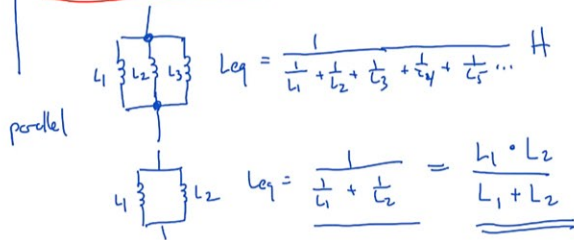
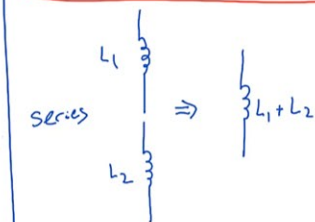
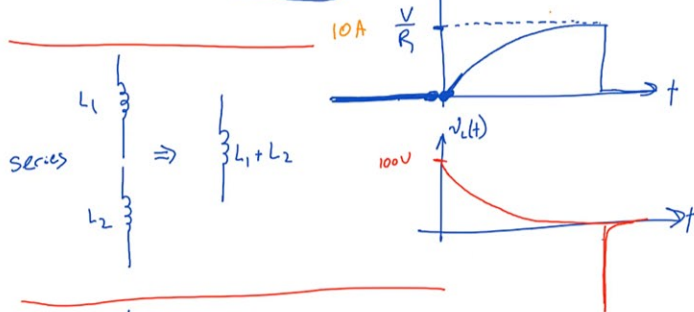



Overview

	Capacitors	Inductors
Symbols	$C = 2\mu F$	$L = 4mH$
intuition	stores energy in electric field diagram	store energy in magnetic field water in a long pipe
tries to keep constant	voltage constant	current constant
math ($p = i \cdot v$ always)	$i = C v'$ $v = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + v(t_0)$ $w = \frac{1}{2} C v^2$	$v = L i'$ $i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$ $w = \frac{1}{2} L i^2$
DC response	$\frac{1}{s} \Rightarrow \frac{b}{a}$	$\frac{1}{s} \Rightarrow \frac{1}{s}$
Construction	$C = \epsilon \frac{A}{d}$	$L = \mu \frac{N^2 A}{l}$
series/parallel	opposite R	same R
opamps	KCL at inputs 	not used

Intuition

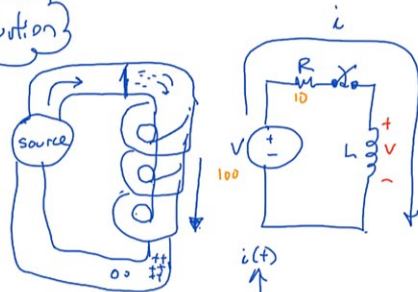

Math

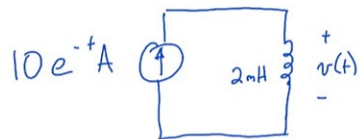

Find $v(t)$


$$v(t) = L i'$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$

$$v(t) = (2m)(-10e^{-t}) V$$

$$= \boxed{-20e^{-t} mV}$$

$$(0.002)(-10e^{-t})$$

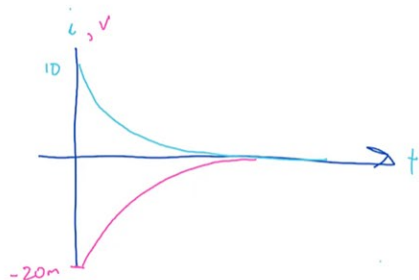

engineering units

10^9 G
 10^6 M
 10^3 k
 10^0 (i)
 10^{-3} m
 10^{-6} μ
 10^{-9} n
 10^{-12} p


$\times$	$\div$
$m \cdot k = l$	$\frac{m}{k} = \mu$
$m M = k$	$\frac{k}{M} = m$
$k k = M$	$\frac{m}{n} = \mu$
$p M = \mu$	

$$(6\mu)(12k) = 72 m$$



$$0.000006 \cdot 12000 =$$

$$6 \times 10^{-6} \times 12 \times 10^3 =$$

DC Response

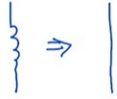

Ex

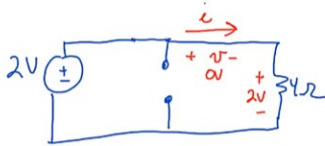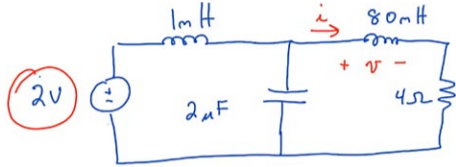


$$i = \frac{V}{R} = \frac{2}{4} = \frac{1}{2} \text{ A}$$
$$V = \boxed{0 \text{ V}}$$

Find energy stored in the 80mH inductor

$$\begin{aligned} W_L &= \frac{1}{2} L i^2 \\ &= \frac{1}{2} (80 \text{ m}) \left(\frac{1}{2} \right)^2 \\ &= \frac{1}{8} (80 \text{ m}) \\ &= \boxed{10 \text{ mJ}} \end{aligned}$$

Construction

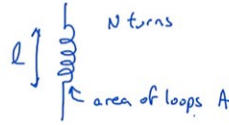

$$L = \mu \frac{N^2 A}{l}$$

↑
constant



Here are some examples of surface mount inductors




Ex

$t > 0$

$$V = L \frac{di}{dt}$$
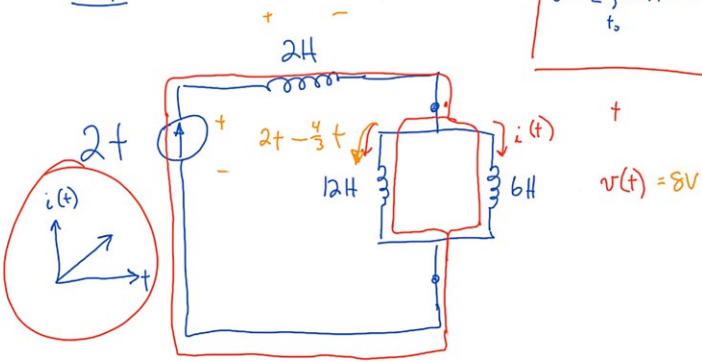
$$i = \frac{1}{L} \int_{t_0}^t v(\tau) d\tau + i(t_0)$$



Find

① $v(t)$


② $w(t)$ in 2H

③ $i(t)$ assuming $i(0) = 0A$

③ ~~$i(t) = 2t$~~




$$V_b = 8V$$
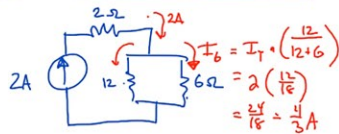
$$i_b = \frac{1}{L} \int_0^t v(\tau) d\tau + i(0) = \frac{1}{6} \int_0^t 8 d\tau + 0 = \frac{1}{6} \cdot 8 \int_0^t d\tau = \frac{4}{3} t A$$



① Can we simplify 12//6?
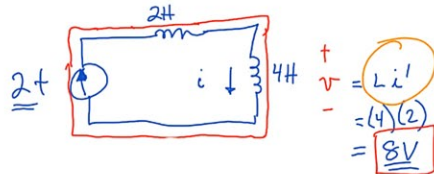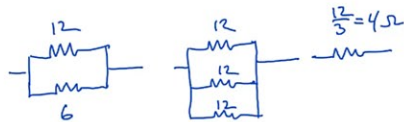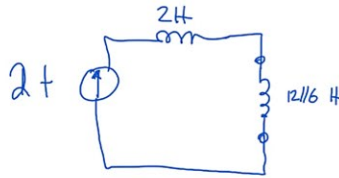
$$12//6 = \frac{1}{\frac{1}{6} + \frac{1}{12}} = \frac{6 \cdot 12}{6 + 12} = 4H$$



② $w(t)$ in 2H $w(t) = \frac{1}{2} L i^2 = \frac{1}{2} (2) (2t)^2 = 4t^2 J$