



1. Find $v(t)$ for all time
2. Find $i_1(t)$ for $t > 0$
3. Find $i_2(t)$ for $t > 0$
4. Roughly, when is cap 99% discharged?
5. Exactly, when cap 50% discharged?