
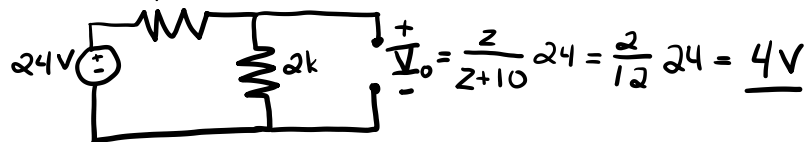


1. Find  $v(t)$  for all time

Before  $t=0$

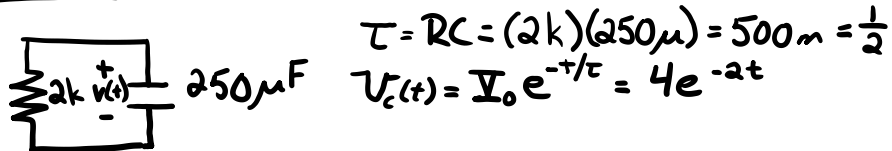

After  $t=0$



$$v(t) = \begin{cases} 4V, & t < 0 \\ 4e^{-2t}, & t \geq 0 \end{cases}$$

2. Find  $i_1(t)$  for  $t > 0$

by  $\Omega$ 's Law,  $i_1(t) = v(t)/2k$

$$= \underline{2e^{-2t} \text{ mA}, t \geq 0}$$

3. Find  $i_2(t)$  for  $t > 0$

by  $i = C v_c'$

$$i_2(t) = C v_c'(t) = (250\mu)(-8e^{-2t}) = -2000e^{-2t} \mu A$$

$$= \underline{-2e^{-2t} \text{ mA}}$$

4. Roughly, when is cap 99% discharged?

$\approx 99\%$  discharged at  $t = 5\tau$

$$= 5(\frac{1}{2}) \approx \underline{2.5 \text{ s}}$$

5. Exactly, when cap 50% discharged?

Exact 50% discharged when  $V = 50\%$  of  $4V = 2V$   
 $Q = 4e^{-2t}$ , solve for  $t$

$$\frac{1}{2} = e^{-2t}$$

$$\ln\left(\frac{1}{2}\right) = -2t \Rightarrow t = -\frac{1}{2} \ln\left(\frac{1}{2}\right) = \boxed{0.347s}$$

check: makes intuitive sense; a little less than  $T = 0.5 \text{ sec}$