



Find

- a) i_L , $t > 0$
- b) i_0 , $t > 0$
- c) v_0 , $t > 0$
- d) percentage of total inductor energy that is dissipated in the 10Ω resistor.

2.) Find $\frac{d}{dt} \{e^{-t} v(t)\}$