
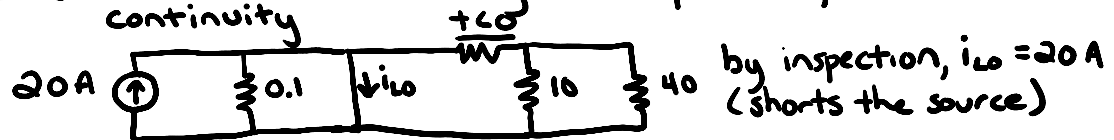


- Circuit is first order and has only DC sources, so use PnC Method.

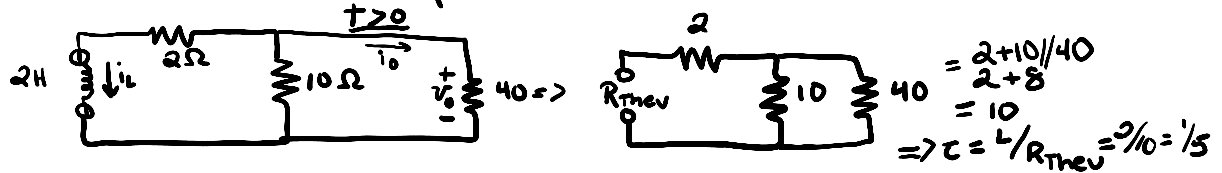Step 1: Find $i_L(t=0)$ by drawing circuit for $t < 0$, current continuity



Step 2: Find τ by redrawing ckt for $t > 0$ and find R_{Th} from L's viewpoint



a) Find: a) i_L , $t > 0$

$$a) i_L(t) = i_L(0)e^{-t/\tau}, t \geq 0$$

$$= 20e^{-5t} A, t > 0$$

Step 3: Use $i_L(t)$ to find any other requested variables

b) i_0 , $t > 0$

b) current divider law applied to the $t > 0$ circuit (note i_L supplies current, divided between the 10Ω and 40Ω resistor)

$$i_0 = -i_L \frac{10}{10+40} = -i_L \frac{1}{5}$$

$$i_0 = -4e^{-5t} A, t > 0$$

c) v_o , $t > 0$

By Ohm's Law,

$$v_o = i_o \cdot 40$$

$$v_o = -160e^{-5t} \text{ V}, t > 0$$

d) percentage of total inductor energy that is dissipated in the 10Ω resistor.

initial energy stored in inductor is $\frac{1}{2}Li^2 = \frac{1}{2}(2)(20)^2 = 400 \text{ J}$

power dissipated in $10\Omega = i_o \cdot v_o = 2560e^{-10t} \text{ W}$

energy dissipated in $10\Omega = \int_0^\infty 2560e^{-10t} dt = 256 \text{ J}$

percentage of total energy diss in $10\Omega = \frac{256}{400} 100\% = 64\%$

2.) Find $\frac{d}{dt} \{e^{-t} v(t)\}$

Method 1: Math

$$\begin{aligned} \frac{d}{dt} \{e^{-t} v(t)\} &= \frac{d}{dt} \{e^{-t}\} v(t) + e^{-t} \frac{d}{dt} \{v(t)\} \\ &= -e^{-t} v(t) + e^{-t} \delta(t) \\ &= -e^{-t} v(t) + \delta(t) \quad (\text{since } \delta(t) \text{ non zero only at } t=0) \end{aligned}$$

Method 2: Graphics

$$\frac{d}{dt} \left\{ \begin{array}{c} \text{graph of } e^{-t} v(t) \end{array} \right\} = \begin{array}{c} \text{graph of } \delta(t) \end{array}$$