


1) Express the following signal in terms of singularity functions, i.e. $u(t)$, $\delta(t)$, $r(t)$. Hint: sketch them first.

a) $v(t) = \begin{cases} 0, & t < 0 \\ -5, & t \geq 0 \end{cases}$



$-5u(t)$

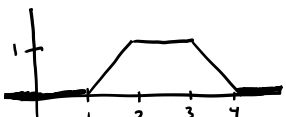
b) $i(t) = \begin{cases} t-1, & 1 < t \leq 2 \\ 1, & 2 < t \leq 3 \\ 4-t, & 3 < t \leq 4 \\ 0, & \text{otherwise} \end{cases}$



$=$




$+$

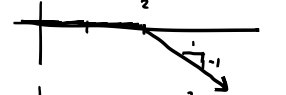

$+$




$+$

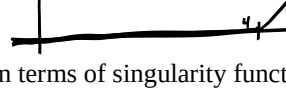

$r(t-1) - r(t-2) - r(t-3) + r(t-4)$

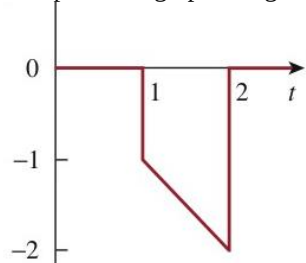
2) Express the graphed signal $v(t)$ in terms of singularity functions.



$=$



$+$

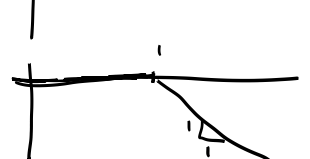

$+$




$+$




$-u(t-1) - r(t-1) + r(t-2) + 2u(t-2)$

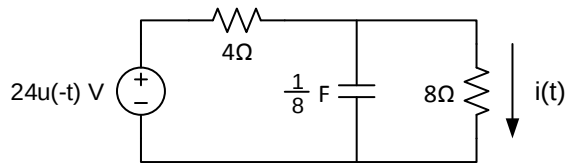
3) Find $i(t)$ for $t \geq 0$ in the circuit below:



① Find V_{co} : $t < 0$ $v(-t) = 1$

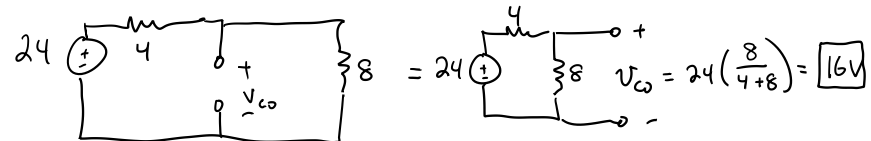

② Find τ : $t \geq 0$ $v(-t) = 0$

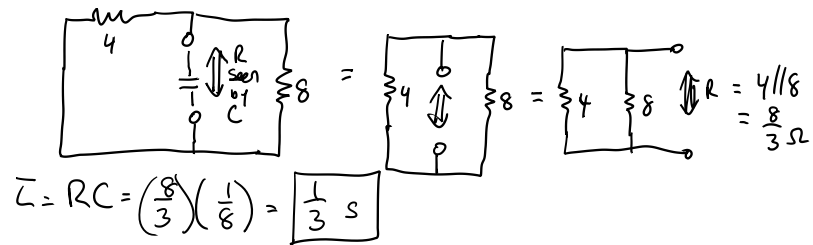

③ Find $v_c(t)$

$$v_c(t) = V_{co} e^{-t/\tau} = 16 e^{-3t}$$

④ Find $i(t)$

$$i(t) = \frac{v_c(t)}{R} = \frac{v_c(t)}{8} = \frac{16 e^{-3t}}{8} = 2 e^{-3t} \text{ A}$$