

**Concept:** First order circuits and opamps

**Find:**  $v(t)$  for **all** time in the following circuit:

