
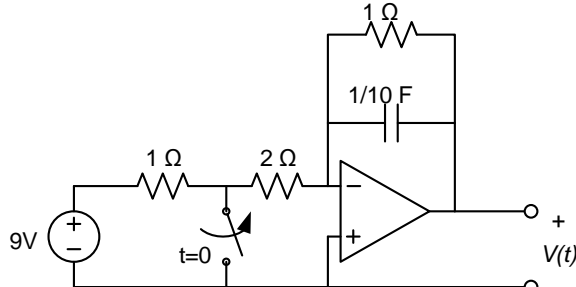


**Concept:** First order circuits and opamps

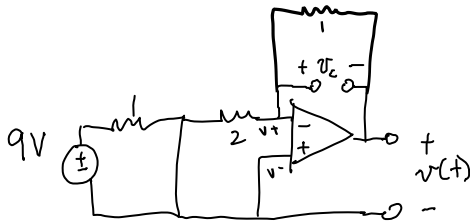**Find:**  $v(t)$  for **all** time in the following circuit:




①  $t < 0$



neg feedback so  $v^+ = v^-$   
 $v^+ = 0$  by inspection so  $v^- = 0$   
 KCL @  $v^-$ :  $\frac{0-0}{2} + \frac{0-v}{1} = 0 \Rightarrow v = 0$   
 $v_c = v^+ - v = 0 - 0 = 0$   
 so  $\boxed{V_0 = 0}$


②  $t = \infty$

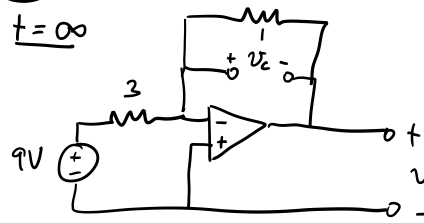

neg feedback so  $v^- = v^+ = 0$   
 KCL @  $v^-$ :  $\frac{0-9}{3} + \frac{0-v}{1} = 0 \Rightarrow v = -3$   
 $v_c = v^- - v = 0 - (-3) = 3$   
 so  $\boxed{V_\infty = 3}$

③  $0 < t < \infty$

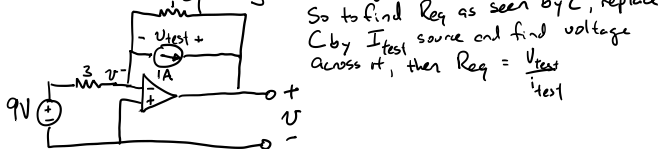Goal: Find  $R_{eq}$  seen by cap. But no indep sources, so must find  $R_{eq}$  using test voltage or current source.



So to find  $R_{eq}$  as seen by C, replace C by  $i_{test}$  source and find voltage across it, then  $R_{eq} = \frac{v_{test}}{i_{test}}$

KCL @  $v^-$ :  $\frac{0-9}{3} + 1 + \frac{0-v}{1} = 0 \Rightarrow v = -2$

$v_{test} = v^- - v = 0 - (-2) = 2V$

$R_{eq} = \frac{v_{test}}{i_{test}} = \frac{2}{1} = 2\Omega$

$\tau = RC = 2\left(\frac{1}{10}\right) = \frac{1}{5} s$

$\boxed{\tau = \frac{1}{5} s}$

④ Sub into PnC equation

$$v_c(t) = V_\infty + (V_0 - V_\infty)e^{-t/\tau}$$

$$= 3 + (0-3)e^{-5t}$$

$$= 3(1-e^{-5t})$$

$$v_c(t) = \begin{cases} 0V, & t < 0 \\ 3(1-e^{-5t}), & t \geq 0 \end{cases}$$

⑤

Find the variable you are asked to find

$$v(t) = v^-(t) - v_c(t)$$

$$= 0 - v_c(t)$$

$$v(t) = \begin{cases} 0V, & t < 0 \\ -3(1-e^{-5t})V, & t \geq 0 \end{cases}$$