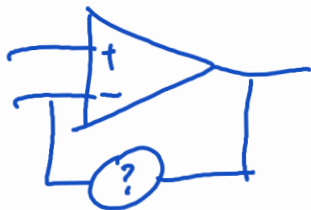


Opamps & 1st order



$$i_c = C v_c'$$

Rules


- $v^+ = v^-$ if neg feedback
- $i^+ = 0, i^- = 0$

Analysis Method

- KCL @ Inputs
- never KCL @ output

Steps 1st order

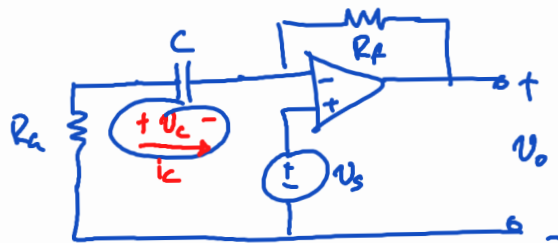
- ① V_{co}, I_{co} $t < 0$ DC steady state
- ② I $t > 0$
- ③ V_{coo}, I_{coo} $t = \infty$ DC steady state
- ④ $v_c = V_{coo} + (V_o - V_{coo})e^{-t/\tau}$
 $i_c = I$
- ⑤ Find asked to find



$$R_a = 20k \quad C = 5\mu F$$

$$R_f = 80k \quad v_s = 3u(t) + 3$$


Find v_o

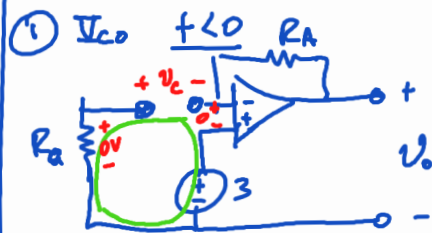

$$\text{KVL: } -0 + v_c + 0 + 3 = 0$$


$$v_c = -3V$$

② $t > 0 \quad \tau = R_{eq} \cdot C$

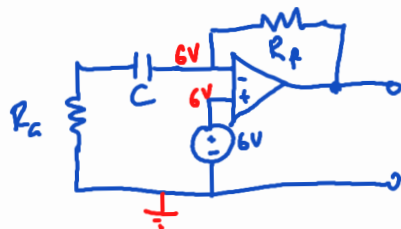

When find $R_{eq} (\tau = R_{eq} \cdot C)$ for opamps

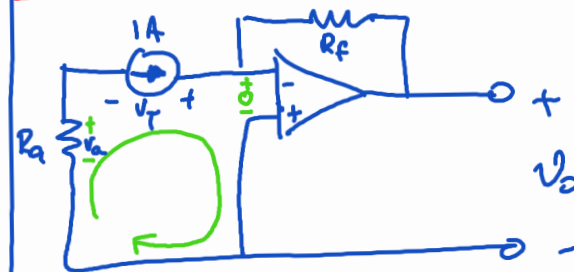- ① Zero all sources
- ② Replace C w/ $I_T = 1A$
- ③ V_T is across $I_T \Rightarrow R_{eq} = \frac{V_T}{I_T} \Rightarrow \tau = R_{eq} \cdot C$



$$\text{KVL: } -V_a - V_T + 0 = 0$$

$$V_a = (-1A)R_a$$

$$\text{KVL: } -R_a - V_T = 0$$

$$V_T = R_a$$

$$R_{eq} = \frac{V_T}{I_T} = \frac{R_a}{1} = R_a$$

$$\tau = R_{eq} \cdot C$$

$$= R_a \cdot C$$

$$= (20k)(5\mu)$$


$$= 100m = 0.1$$

$$\tau = 10$$


$$t/\tau$$

$$+ / 100m$$

$$+ / (1/10) = 10t$$

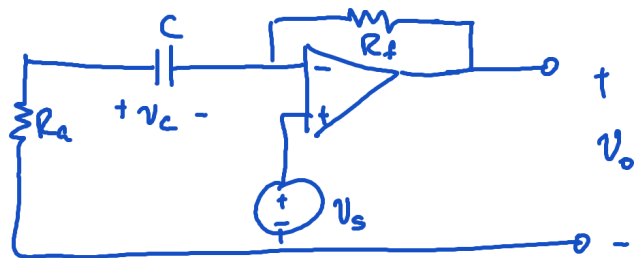

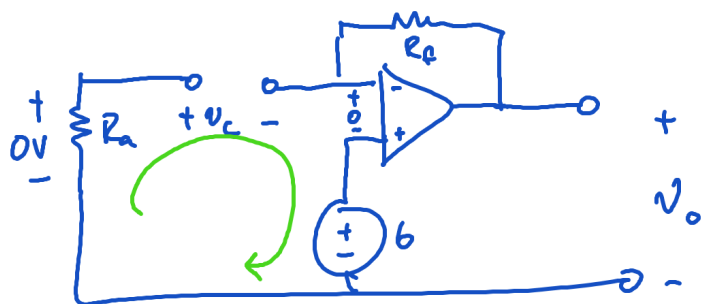
③ Find $V_{c\infty}$ $t=\infty$ DC steady state



KVL given: $-0 + v_c + 0 + 6 = 0$



$V_{c\infty} = -6V$

$3u(t) + 3$

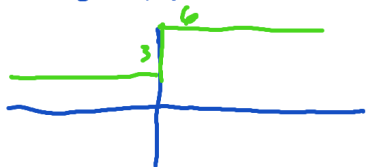

④ $v_c(t) = V_{\infty} + (V_0 - V_{\infty})e^{-t/\tau}$
 $= -6 + (-3 - (-6))e^{-t/(4/10)}$
 $= -6 + 3e^{-10t} V, t \geq 0$

⑤

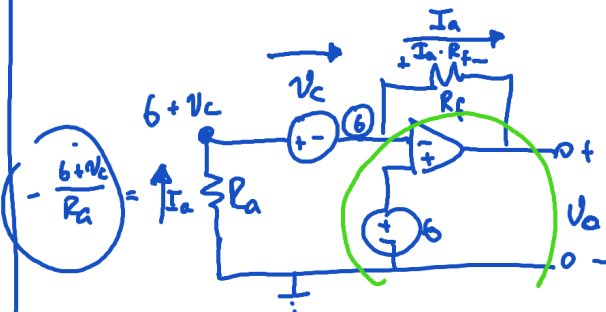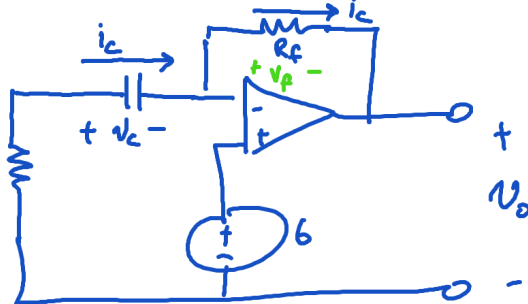

$V_f = I_a \cdot R_f$

KVL: $-6 + 0 + V_f + V_o = 0$
 $V_o = 6 - V_f$
 $= 6 - I_a R_f$

$V_o = 6 - (-\frac{6+v_c}{R_a}) R_f$
 $= 6 + \frac{R_f}{R_a} (6 + v_c)$
 $= 6 + 4(3e^{-10t})$
 $= 6 + 12e^{-10t} V$

$i_c = C v_c'$
 $= (5\mu)(-30e^{-10t}) A$
 $= -150\mu e^{-10t} A$
 $= -150e^{-10t} \mu A$

$V_f = R_f \cdot i_c$
 $= (80k)(-150e^{-10t}) \mu$
 $= -1200e^{-10t} m$
 $= -12e^{-10t} V$

$V_o =$

$-6 + 0 + V_f + V_o = 0$
 $-6 - 12e^{-10t} + V_o = 0$
 $V_o = 6 + 12e^{-10t} V$