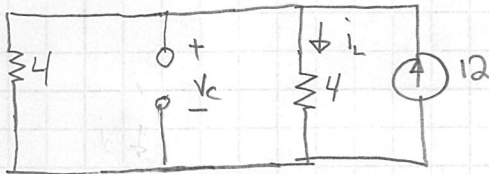


Find

$$\begin{array}{ll} V_c(0^+) & V_c'(0^+) \\ i_L(0^+) & i_L'(0^+) \\ V_2(0^+) & V_2'(0^+) \\ V_L(0^+) & V_L'(0^+) \end{array}$$


① Draw $t < 0$, find i_L , V_c always. $\frac{1}{s} \Rightarrow \frac{1}{s}$ $\frac{1}{s} \Rightarrow 1$



$$i_L = 12 \frac{4}{4+4} = 6A \quad \text{divider}$$

$$V_c = 4 \cdot i_L = 24V \quad \Omega\text{'s Law}$$

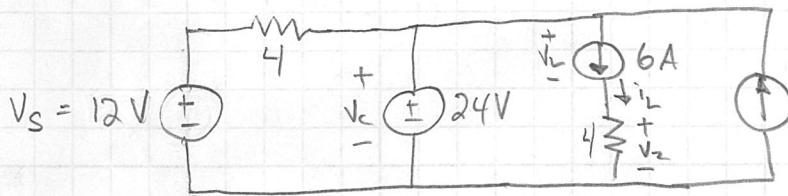② Draw $t = 0^+$, find whatever asked to find. $\frac{1}{s} \Rightarrow \oplus$ $\frac{1}{s} \Rightarrow \oplus$



$$\begin{array}{l} V_c(0^+) = 24V \quad \text{by inspection - directly across a voltage source} \\ i_L(0^+) = 6A \quad \text{by inspection - directly through a current source} \\ V_2(0^+) = (6A)(4\Omega) = 24V \quad \text{by } \Omega\text{'s Law} \end{array}$$

$$V_c'(0^+): i_c = C V_c' \Rightarrow V_c' = \frac{1}{C} i_c$$

$$\begin{array}{l} = (5)(3) \\ = 15V/s \end{array}$$

$$\text{To find } i_c: \text{KCL top right: } \frac{24-12}{4} + i_c + 6 - 12 \Rightarrow i_c = 3A$$

$$i_L'(0^+): V_L = L i_L' \Rightarrow i_L' = \frac{1}{L} V_L$$

$$\begin{array}{l} = \frac{1}{2}(0) \\ = 0A/s \end{array}$$

$$\text{To find } V_L: \text{KVL middle loop: } 24 - V_2 - V_L = 0 \Rightarrow V_L = 0V \text{ since } V_2 = 24 \text{ above}$$

$$V_2'(0^+): V_2 = i_L \cdot 4$$

$$\begin{array}{l} V_2' = i_L' \cdot 4 \\ = 0 \cdot 4 \\ = 0V/s \end{array}$$

$$\Omega\text{'s Law and } i_L = i_4$$

$$\text{take deriv. both sides}$$

$$i_L' \text{ found above}$$

$$V_L'(0^+): \text{KVL middle loop: } V_c - V_2 - V_L = 0$$

$$\begin{array}{l} V_L = V_c - V_2 \\ V_L' = V_c' - V_2' \\ = 15 - 0 \\ = 15V/s \end{array}$$

$$\text{Solve for } V_L$$

$$\text{Take deriv of eqn}$$

$$V_c', V_2' \text{ found above}$$

Summary

$$\begin{array}{ll} V_c(0^+) = 24V & V_c'(0^+) = 15V/s \\ i_L(0^+) = 6A & i_L'(0^+) = 0A/s \\ V_2(0^+) = 24V & V_2'(0^+) = 0V/s \\ V_L(0^+) = 0V & V_L'(0^+) = 15V/s \end{array}$$