
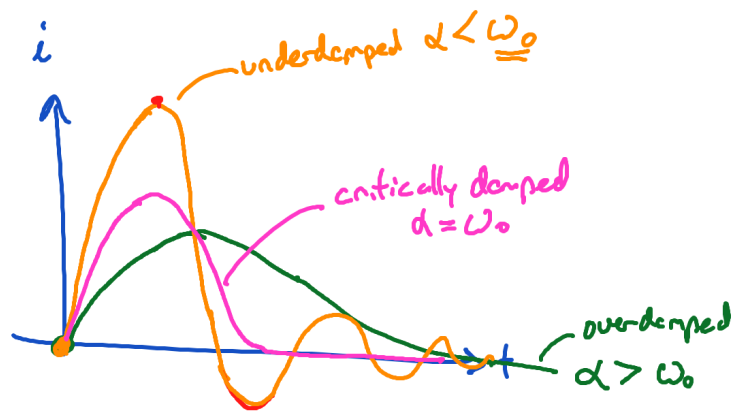
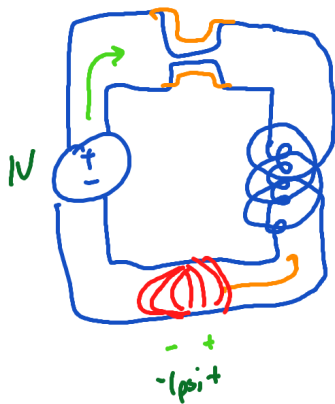


Intuition

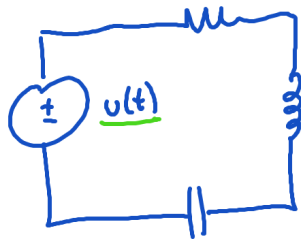

Big Picture

2nd order circuit
2 energy storage elements

step input
= switched DC
RLC series or parallel

Sinusoids

anything

PnC
= Test 2 block

Phasors
= Test 3 block

Laplace
EE230

15, 16

no source

17, 18

source

Review

① Calc - DSC "Disc"

$$\frac{d}{dt} \sin(2t) = 2 \cos 2t$$

$$\frac{d}{dt} \cos(2t) = -2 \sin 2t$$

② Product rule


$$[f(t) \cdot g(t)]' = f'(t)g(t) + f(t)g'(t)$$

③

$$v_L = L i_L'$$

$$i_C = C v_C'$$


Ex

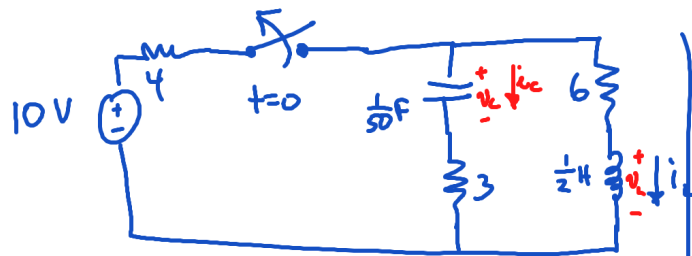

Find i_L

① Find IC

(a) $t < 0$ i_L, v_C

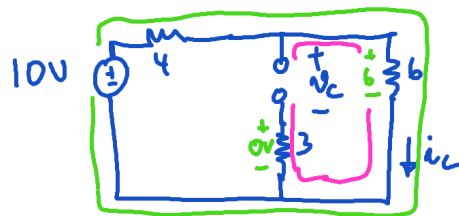


$$i_L = \frac{10V}{4+6} = 1A$$

$$v_C = 6V$$

(b) $t = 0^+$

$$i_L(0^+) = 1A$$

$$i_L'(0^+) = -6A/s$$

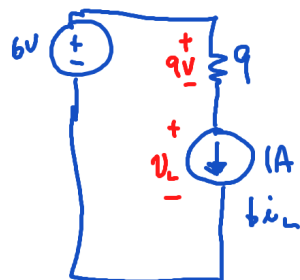

$$-6 + 9 + v_L = 0$$

$$v_L = -3V$$

$$i_L = C v_C'$$

$$v_L = L i_L'$$


$$i_L'(0^+) = \frac{1}{L} v_L(0^+)$$

$$= \frac{1}{2} (-3)$$

$$= -1.5 A/s$$

$$\frac{d}{dt} i(t) = A/s$$

② $t > 0$ natural solution $i_n(t)$

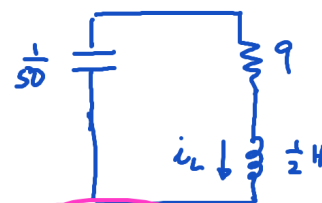

$$\alpha = \frac{R}{2L} = 9$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 10$$

$$S = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$= -9 \pm j4.36$$

$\alpha < \omega_0$ ← underdamped = oscillatory

$$\alpha = \omega_0$$

$$\alpha > \omega_0$$

$$i_n(t) = e^{-\alpha t} [C_1 \cos(\omega_d t) + C_2 \sin(\omega_d t)]$$

$$i_L = e^{-9t} [C_1 \cos(4.36t) + C_2 \sin(4.36t)]$$

$$1 = 1 [C_1 + 0] \Rightarrow C_1 = 1$$

$$i_L = e^{-9t} [\cos(4.36t) + C_2 \sin(4.36t)]$$

$$-6 = -9e^0 [1 + 0] + 1 [-4.36 \sin(0) + 4.36 C_2 \cos(0)]$$

$$-6 = -9 + 4.36 C_2$$

$$C_2 = 0.688$$

$$i_L = e^{-9t} [\cos(4.36t) + 0.688 \sin(4.36t)] A$$

③ $t = \infty$ forced solution $i_f(t)$

$$i_f(\infty) = 0$$

homogeneous = natural
particular = forced

$$i_L = i_n + i_f \quad DSC$$