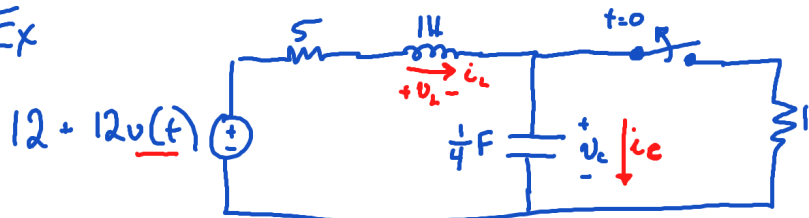


Ex




Find  $v_C$ , all time

① Find IC

②  $t < 0$

$$\begin{cases} i_L \\ v_C \end{cases}$$

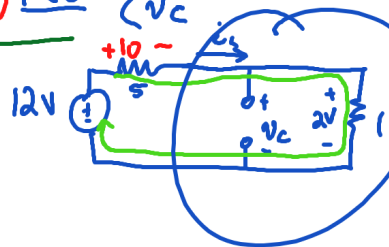

$$\begin{aligned} i_C &= C v_C' \\ v_L &= L i_L' \end{aligned}$$

$$i_L = \frac{V}{R} = 2A \quad \frac{12}{6} = 2A$$

$$v_C = 12 \cdot \frac{1}{s+1} = 2V$$

$$v_C = 2V \quad (2A)(1\Omega) = 2V$$

③  $t = 0^+$

$$\begin{cases} x \\ x' \end{cases} \quad \begin{aligned} v_C &= 2V \\ v_C' &= 8V/s \end{aligned}$$



$$\begin{aligned} v_C' &= \pm i_C \\ &= 4(2) \\ &= 8V/s \end{aligned}$$

②  $v_n = x_n$

$$\alpha = \frac{R}{2L} = 2.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = 2$$

$$s = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = \{-1, -4\}$$

$\omega_d = \sqrt{\omega_0^2 - \alpha^2}$  not osc over damp

$\alpha = \omega_0$  " critically damp

$\alpha < \omega_0$  oscil underdamped

$t > 0$




$$v_n(t) = c_1 e^{s_1 t} + c_2 e^{s_2 t} \leftarrow \text{overd.}$$

$$v_n(t) = c_1 e^{st} + c_2 t e^{st} \leftarrow \text{crit.}$$

$$v_n(t) = e^{-\alpha t} [c_1 \cos(\omega_d t) + c_2 \sin(\omega_d t)] \leftarrow \text{underd.}$$

$$v_n = c_1 e^{-t} + c_2 e^{-4t}$$

③  $v_f = x_f$

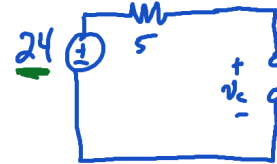

$$v_f = 24V$$

$$x = x_n + x_f$$

④  $v_C(t) = v_n + v_f$ , sub IC

$$v_C(t) = c_1 e^{-t} + c_2 e^{-4t} + 24$$

$$v_C(0) = 2 = c_1 + c_2 + 24 \Rightarrow c_1 + c_2 = -22$$

$$v_C'(0) = 8 = -c_1 - 4c_2 \Rightarrow c_1 - 4c_2 = 8$$

$$-3c_2 = -14$$

$$c_2 = 14/3 = 4.67$$

$$\begin{aligned} c_1 &= -22 - c_2 \\ &= -22 - 14/3 \\ &= -26.7 \end{aligned}$$

$$v_C(t) = \begin{cases} 2V & t < 0 \\ -26.7 e^{-t} + 4.67 e^{-4t} + 24V & t > 0 \end{cases}$$

$$v_C(t) = 2 + (22)v(t)$$

$$v_C'(t) = -c_1 e^{-t} - 4c_2 e^{-4t}$$

$$v_C'(0) = -c_1 - 4c_2 = 8$$