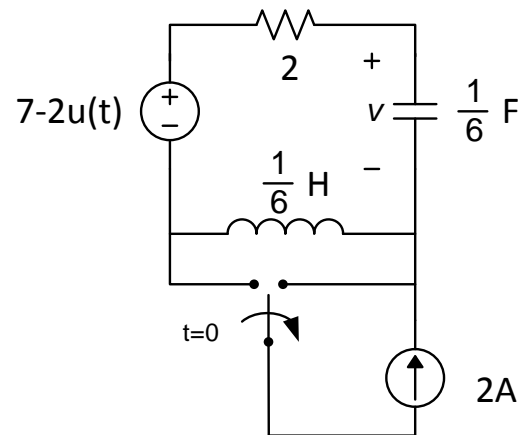


- 1) Find  $v(t)$



- 2) Find  $v(t)$  (circuit similar to the above but solution will look quite different)

