
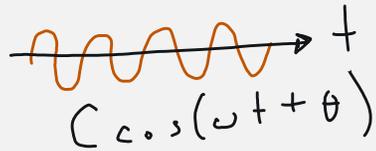
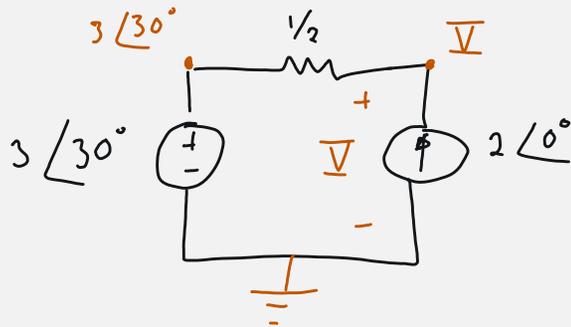
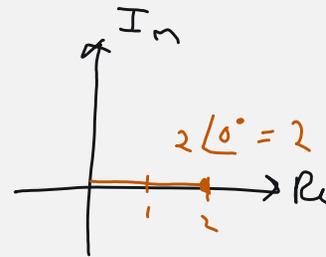
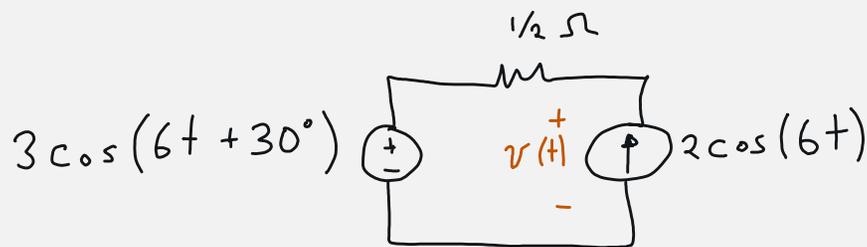


Phasors

Complex number $z = C \angle \theta$ representing sinusoid

 $C \cos(\omega t + \theta)$

$$z = C \angle \theta$$

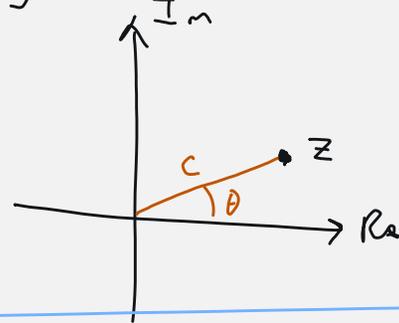

$$V : \frac{V - 3 \angle 30^\circ}{1/2} + (-2) = 0$$

$$2V - 6 \angle 30^\circ - 2 = 0$$

$$2V = 6 \angle 30^\circ + 2$$

$$V = 3 \angle 30^\circ + 1$$

$$= (3 \angle 30) + 1 \leftarrow \text{TI calculator}$$

$$= 3.9 \angle 23^\circ$$


Mode
complex: polar
angle: degrees

$$v(t) = 3.9 \cos(6t + 23^\circ) V$$

element	impedance Z	admittance
	$R \Omega$	$\frac{1}{R} S$
	$j\omega L \Omega$	$\frac{1}{j\omega L} S$
	$\frac{1}{j\omega C} \Omega$	$j\omega C S$

Theory

$\cos(\omega t)$

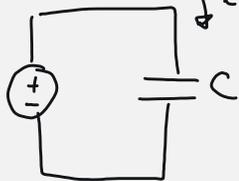

$$\begin{aligned}
 i(t) &= C v'(t) \\
 &= C \cdot \cos'(\omega t) \\
 &= -C\omega \sin(\omega t) \\
 &= -C\omega \cos(\omega t - 90^\circ)
 \end{aligned}$$

$$I \Rightarrow -C\omega \angle -90^\circ$$

$$\begin{aligned}
 Z &= \frac{V}{I} = \frac{1}{-C\omega \angle -90^\circ} \\
 &= \frac{1 \angle 0^\circ}{-C\omega \angle -90^\circ}
 \end{aligned}$$


$$= \frac{1}{-C\omega} \angle 90^\circ$$

$$= -\frac{j}{C\omega}$$

$$= \boxed{\frac{1}{j\omega C}}$$


$$\frac{A \angle \theta_1}{B \angle \theta_2} = \frac{A}{B} \angle (\theta_1 - \theta_2)$$
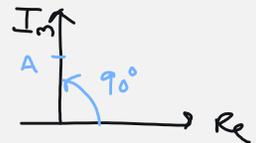
$$\begin{aligned}
 A \angle 90^\circ \\
 = jA
 \end{aligned}$$




$$\frac{1}{j} \cdot \frac{j}{j} = \frac{j}{j^2} = \frac{j}{-1} = -j$$

Ex

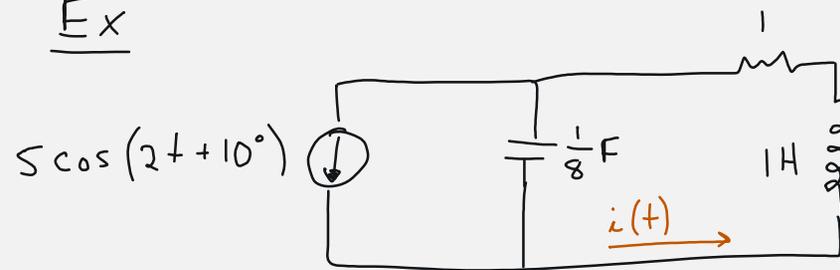

① Convert to phasor domain

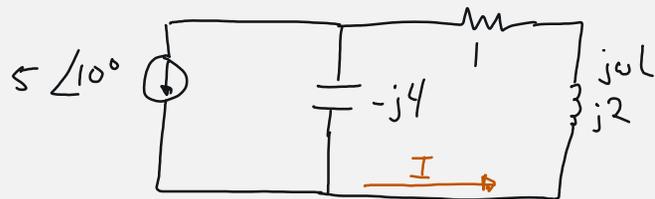

② Analyze DC methods

$$I = \left(5 \angle 10^\circ \frac{-j4}{-j4 + 1 + j2} \right) = 8.94 \angle -16.5^\circ$$

③

$$i(t) = 8.94 \cos(2t - 16.5^\circ) \text{ A}$$

$$Z_c = \frac{1}{j\omega C} = \frac{1}{j(2)(\frac{1}{8})} = \frac{1}{j\frac{1}{4}} = \frac{4}{j} = -j4$$

$$\frac{1}{j} \cdot \frac{j}{j} = \frac{j}{j^2} = \frac{j}{-1} = -j \quad \begin{array}{l} j = \sqrt{-1} \\ j^2 = -1 \end{array}$$

$$\boxed{\frac{1}{j} = -j}$$