
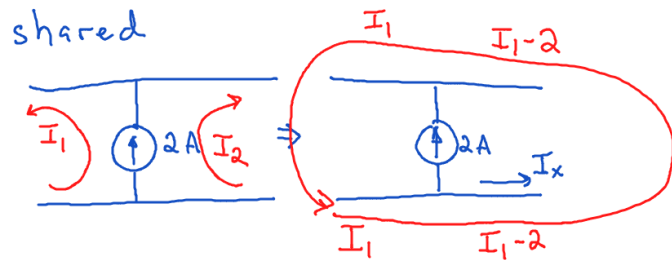


Phasors & Mesh organized KVL



$$\sum_{\text{mesh}} V_{\text{is}} = 0$$

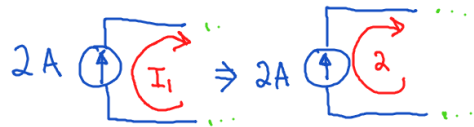- ① Create I_1, I_2 etc variables direction
- ② For each I_{source} , reduce 1 unknown not shared



③ Dep? Extra eqn

④ Matrix

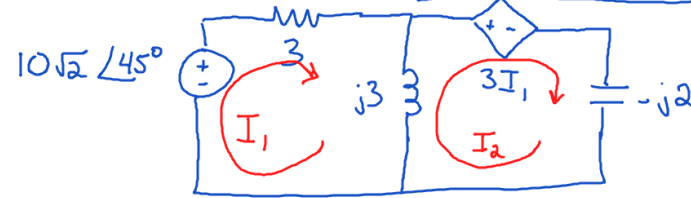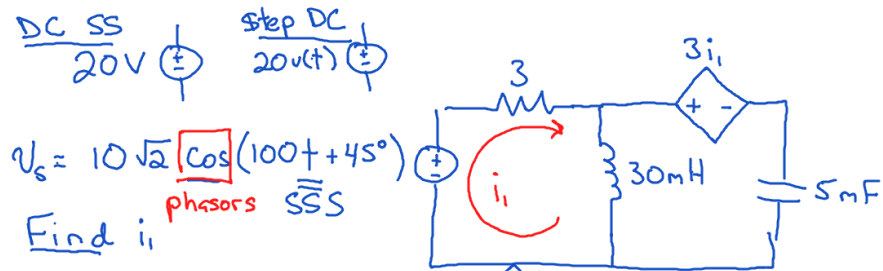

$$Z_L = j\omega L = j100(30m) = j3000m = j3$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j100 \cdot 5m} = \frac{-j}{0.5} = -j2$$

$$I_1: -10\sqrt{2} \angle 45^\circ + 3I_1 + j3(I_1 - I_2) = 0$$

$$I_1(3 + j3) + I_2(-j3) = 10\sqrt{2} \angle 45^\circ$$

$$I_2: j3(I_2 - I_1) + 3I_1 - j2I_2 = 0$$


$$I_1(3 - j3) + I_2(j3 - j2 = j) = 0$$

$$\begin{bmatrix} 3 + j3 & -j3 \\ 3 - j3 & j \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10\sqrt{2} \angle 45^\circ \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 1.05 \angle 71.6^\circ \\ \sim \end{bmatrix}$$

$$i_1(t) = 1.05 \cos(100t + 71.6^\circ)$$



Ex

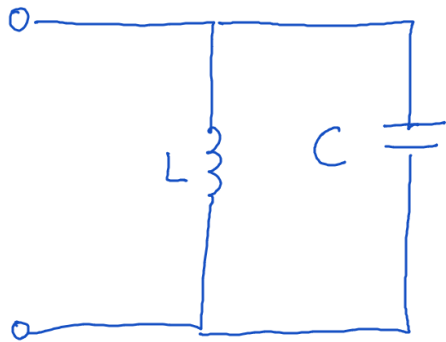

a) Is there any freq at which this ckt looks like a wire? (what freq?)

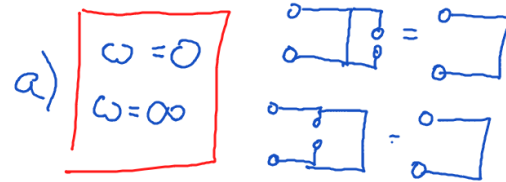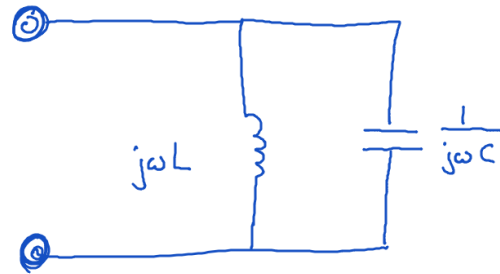b) Is there any freq at which this ckt looks like an open? (what freq?)

$$j = \sqrt{-1} \quad \frac{1}{j} = -j$$
$$j^2 = -1$$



b)

$$Z = j\omega L \parallel \frac{1}{j\omega C}$$
$$= \frac{j\omega L}{j\omega C} \cdot \frac{j\omega C}{j\omega L + \frac{1}{j\omega C}}$$
$$= \frac{j\omega L}{j^2 \omega^2 LC + 1}$$
$$= \left[\frac{j\omega L}{1 - \omega^2 LC} \right]$$


$$1 = \omega^2 LC$$

$$\omega^2 = \frac{1}{LC}$$

$\omega = \frac{1}{\sqrt{LC}}$

Ex

Find I_0

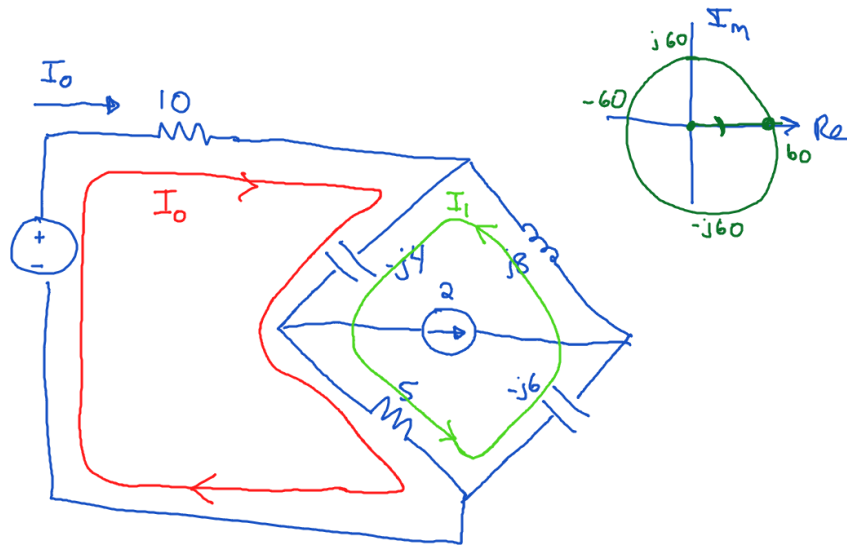

$$I_0 : -60 + 10I_0 + -j4(I_0 + I_1) + 5(I_0 + I_1) = 0$$

$$I_0(15 - j4) + I_1(5 - j4) = 60$$

$$I_1 : -j4(I_0 + I_1) + 5(I_0 + I_1) - j6I_1 + j8I_1 = 0$$

$$I_0(5 - j4) + I_1(5 - j4 - j6 + j8) = 0$$

$$I_0(5 - j4) + I_1(5 - j2) = 0$$

$$\begin{bmatrix} 15 - j4 & 5 - j4 \\ 5 - j4 & 5 - j2 \end{bmatrix} \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 60 \\ 0 \end{bmatrix} \quad \begin{bmatrix} I_0 \\ I_1 \end{bmatrix} = \begin{bmatrix} 5.95 \angle 3.2^\circ \\ 4.34 \angle 176^\circ \end{bmatrix}$$

$$I_0 = 5.95 \angle 3.2^\circ \text{ A}$$

$$Z_{eq} = \frac{V}{I} = \frac{60 \angle 0^\circ}{5.95 \angle 3.2^\circ} = \frac{60}{5.95} \angle -3.2^\circ$$