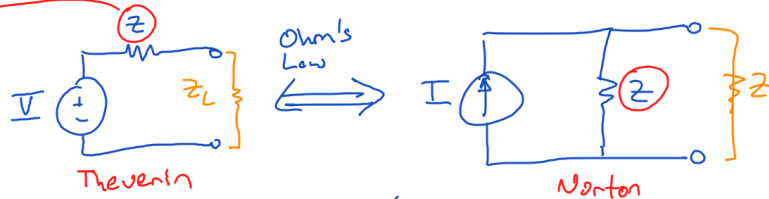



Phasors

- source transforms
- superposition


Source Transforms



Degenerate

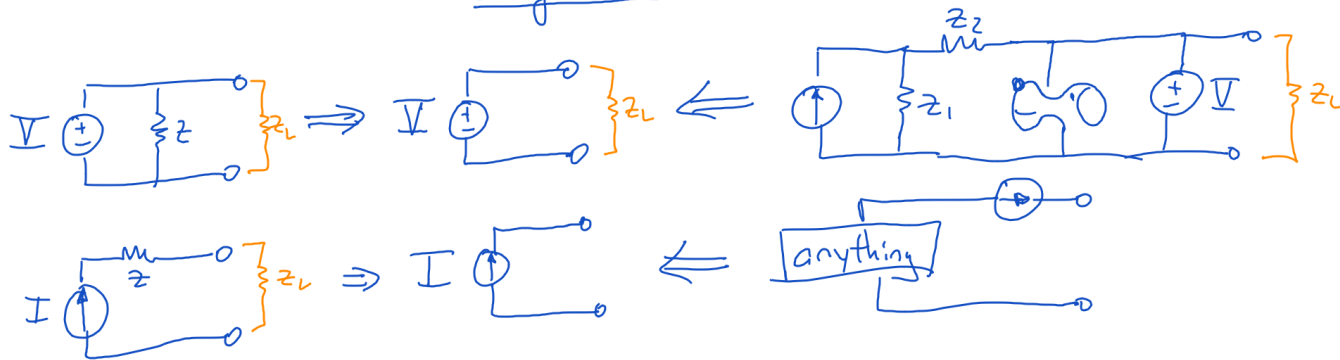

Ex Find the equiv of

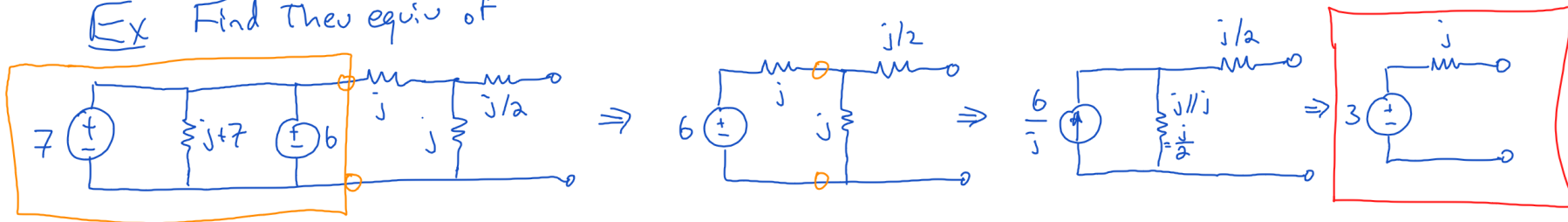

Superposition

- Zero all indep sources but 1
(keep all dep sources on)
- If all sources same $\omega \Rightarrow$ add parts in freq domain } one ω
Then convert to time domain
- If sources have different ω 's $\Rightarrow$ convert each phasor to time } lots ω
Then add

Ex

Indep sources: 16V

Partial output: 2V



$$\begin{array}{cc} 5 \cos(\underline{10t} - 53^\circ) \text{V} & 14 \cos(\underline{10t} + 6^\circ) \text{A} \\ \downarrow & \downarrow \\ 2 \angle 30^\circ \text{V} & 1 \angle -10^\circ \text{V} \\ \underbrace{\hspace{10em}} & \\ \underline{2.84 \angle 17^\circ} & \end{array}$$

$$\text{Time } v(t) = 2 + 2.84 \cos(10t + 17^\circ) +$$



$$\begin{array}{c} 5 \sin(\underline{20t}) \text{A} \\ \downarrow \\ \underline{5 \angle 60^\circ} \end{array}$$

$$5 \cos(20t + 60^\circ)$$

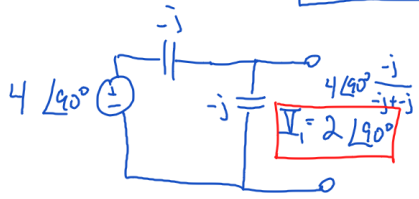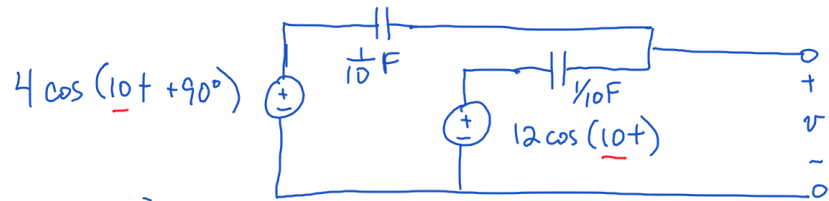Ex: Superposition in Freq domain - Same frequencies



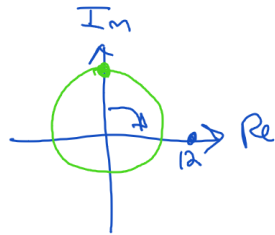
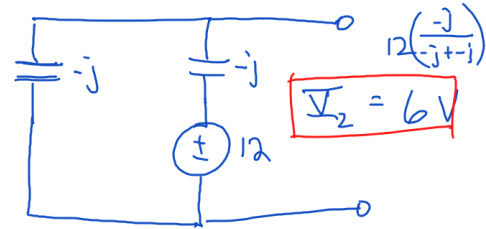
$$Z_C = \frac{1}{j\omega C} = \frac{1}{j10 \cdot \frac{1}{10}} = \frac{1}{j} = -j$$




$$\begin{aligned} V &= 2 \angle 90^\circ + 6 \\ &= j2 + 6 \\ &= 6.32 \angle 18^\circ \end{aligned}$$

$$v(t) = 6.32 \cos(10t + 18^\circ) \text{ V}$$

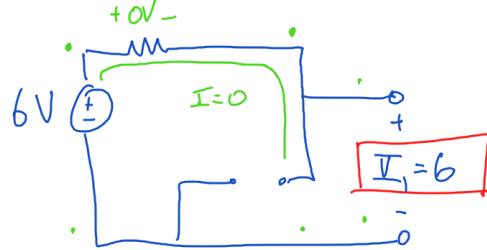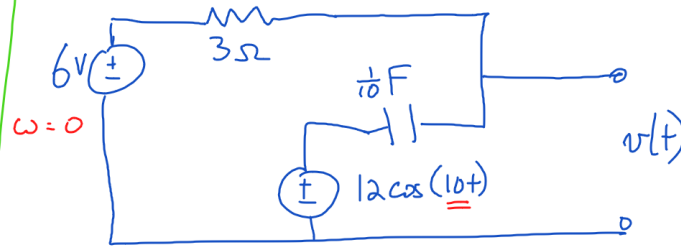Ex: Superposition in Freq Domain - Different freqs


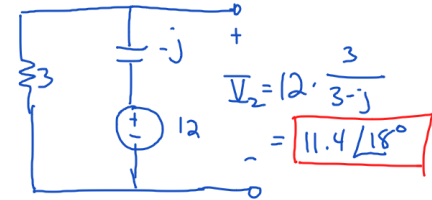
$$\begin{aligned} Z_C &= \frac{1}{j\omega C} = \frac{1}{j10 \cdot \frac{1}{10}} = \infty \\ v_1(t) &= 6 \text{ V} \end{aligned}$$




$$v_2(t) = 11.4 \cos(10t + 18^\circ)$$


$$v(t) = 6 + 11.4 \cos(10t + 18^\circ) \text{ V}$$

Real World

$$EKG = ECG$$

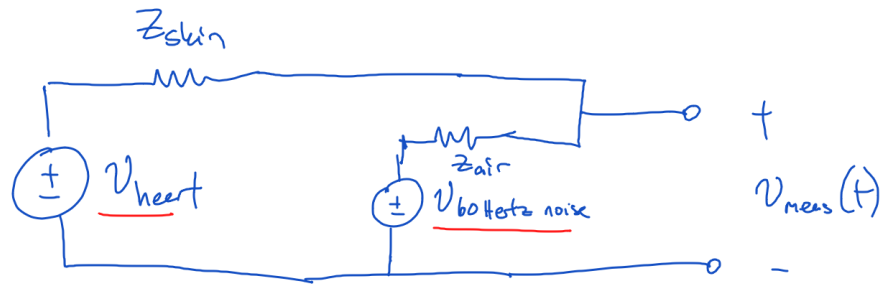

1. Using superposition, find $i(t)$

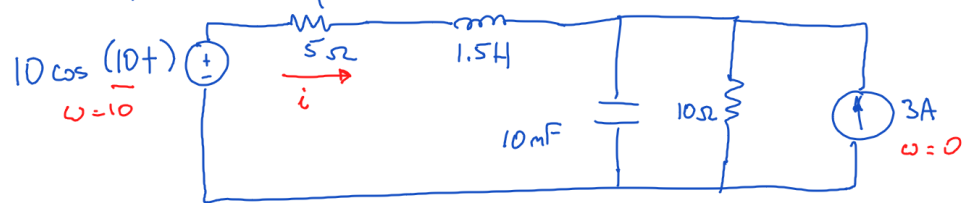

Left On $\omega = 10$

$$Z_L = j\omega L = j15 \Omega$$

$$Z_C = \frac{1}{j\omega C} = \frac{1}{j1000} = -j10 \Omega$$



$$Z_{eq} = (5 + j15) + (-j10 \parallel 10)$$

$$= 5 + j15 + \frac{-j100}{10 - j10}$$

$$= 14.1 \angle 45^\circ \Omega$$

$$I = \frac{V}{Z_{eq}} = \frac{10}{14.1 \angle 45^\circ} = 0.707 \angle -45^\circ$$


$$i_1(t) = 0.707 \cos(10t - 45^\circ) \text{ A}$$

$$i(t) = 0.707 \cos(10t - 45^\circ) - 2 \text{ A}$$

Right On $\omega = 0$

$$Z_L = j\omega L = 0$$

$$Z_C = \frac{1}{j\omega C} = \infty$$

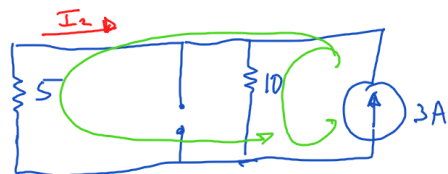


$$I_2 = -\left(3\right) \frac{10}{5+10}$$

$$= -2 \text{ A}$$

$$i_2(t) = -2 \text{ A}$$

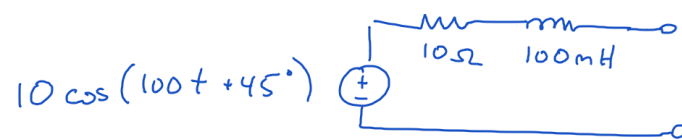2. Find the Norton equivalent of the circuit below in the frequency domain




$$Z_L = j\omega L$$

$$= j100(0.1)$$

$$= j10$$



Thev. equiv.

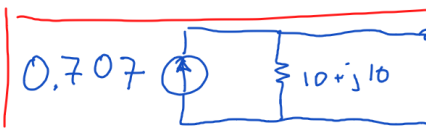

Norton equiv.

$$Z_L = j\omega L$$

$$j10 = j100 \cdot L$$

$$L = \frac{1}{10} \text{ H} = 100 \text{ mH}$$

$$Z_C = \frac{1}{j\omega C} = \frac{-j}{\omega C}$$

