

**P1** If  $v(t) = 160 \cos 50t$  V and  $i(t) = -20 \sin(50t - 30^\circ)$  A, calculate the

- a) **Instantaneous power.** Simplify the product of sinusoids to a single sinusoid plus a constant term.

**Hint:** there is a +800 in the answer

- b) **Average power.**

**Hint:** between 500W and 1kW

**P2** **Concept:** phasors and power analysis

**Find:** In the circuit below,  $i_s = 3\cos(10^3t)$  A. Find the average power absorbed by the 50- $\Omega$  resistor.

**Hint:** First digit of answer is a 6.

You can use mesh (make the two currents  $i_s$  and  $i_x$ , so the right loop is a function of these two; this way you don't introduce extra variables) or nodal analysis. Either way there's only one standard equation plus one for the dependent source. I use nodal in the solutions.

