


P1 Concept: Maximum Average Power Transfer

Find: In the circuit below find

- load impedance Z_L for maximum average power transfer to Z_L
- maximum average power P absorbed by Z_L

Hints:

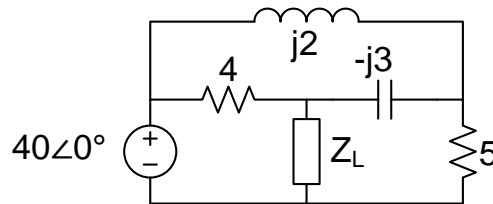- Could use a few different methods for part b; try using nodal analysis
- first digit of real and imaginary parts of Z both 8. First digit of P is 2



P2 Concept: Root Mean Square

Find: Find V_{RMS} of $v(t)$ given below.

Hints:

- It is NOT SSS so can't use $V_{RMS} = V_M/\sqrt{2}$ shortcut
- Looks like a scaled cos wave plus a constant
- Know $\cos^2(x) = \frac{1}{2} + \frac{1}{2}\cos(2x)$
- You should have a rough "gut" feeling of what the equivalent DC would have to be to generate same power...roughly 2 or $3V_{RMS}$
- Don't forget: units are not V but V_{RMS}

