

Obj

Review

Apparent Power

Power Factor

Leading / Lagging Power

Read

11.5 (11.6)

HW

PS 34 (not collected)

Leading / lagging

$\theta_I > \theta_V$ leading pf = capacitive

$\theta_I < \theta_V$ lagging pf = inductive

$\theta_I = \theta_V$ pf = resistive

Last Time

Notation example : let $v(t) = 10 \cos(3t + 40^\circ)$

then $V_m = 10$ $\theta_V = 40$ $\mathbf{V} = 10 \angle 40^\circ$ $\mathbf{V}^* = 10 \angle -40^\circ$

$V_{RMS} = \frac{10}{\sqrt{2}} V_{RMS}$ $\mathbf{V}_{RMS} = \frac{10}{\sqrt{2}} \angle 40^\circ V_{RMS}$

Average Power = $\frac{1}{T} \int_0^T p(t) dt$ any waveform


$$\begin{aligned} &= \frac{1}{2} V_m I_m \cos(\theta_V - \theta_I) = \frac{1}{2} \operatorname{Re}\{\mathbf{V} \cdot \mathbf{I}^*\} \\ &= V_{RMS} I_{RMS} \cos(\theta_V - \theta_I) = \operatorname{Re}\{\mathbf{V}_{RMS} \cdot \mathbf{I}_{RMS}^*\} \end{aligned}$$

sinusoids only
any component RLC
 $\rightarrow V_{RMS} = \frac{V_m}{\sqrt{2}}$

$$= \underbrace{S}_{\text{apparent power}} \cdot \underbrace{\cos(\theta_V - \theta_I)}_{\text{power factor}}$$

Apparent Power • measured in VA not W
 $\uparrow$ instantaneous power
 $\uparrow$ average power
 $\uparrow$ apparent power

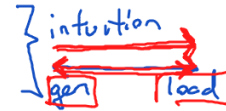- $S = V_{RMS} \cdot I_{RMS}$
- scalar, not a phasor
- $P_{ave} = 0$ for C, L
 $S \neq 0$ for C, L
- what the power company charges you!



Power Factor pf

- $\cos(\theta_V - \theta_I) = \cos(\theta_I - \theta_V)$
- 1 for purely resistive load, 0 for purely inductive or capacitive
- $P_{ave} = S \cdot pf$
 $\uparrow$ what you can use
 $\uparrow$ what you are charged for

Example

across load $v(t) = 120 \cos(2\pi 60t - 20^\circ) V_{\text{rms}}$
 $i(t) = 4 \cos(2\pi 60t + 10^\circ) A_{\text{rms}}$

analyze

- voltage measured in Volts?

$$v(t) = 120\sqrt{2} \cos(2\pi 60t - 20^\circ) V$$

$$i(t) = 4\sqrt{2} \cos(2\pi 60t + 10^\circ) A$$


- apparent power $= S = V_{\text{rms}} \cdot I_{\text{rms}} = \underbrace{120}_{V_{\text{rms}}} \cdot \underbrace{4}_{A_{\text{rms}}} = 480 \text{ VA}$

- $\text{pf} = \cos(\theta_I - \theta_V) = \cos(10 - (-20)) = \cos(30^\circ) = 0.866, \text{ leading}$

- leading or lagging? $\theta_I > \theta_V$
 $10^\circ > -20^\circ$


- $P_{\text{ave}} = S \cdot \text{pf} = \overset{\text{leading}}{(480)(0.866)} = 417 \text{ W}$

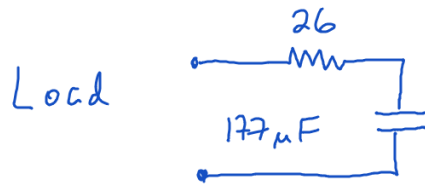- Load impedance $Z = \frac{V_{\text{rms}}}{I_{\text{rms}}} = \frac{120 \angle -20^\circ}{4 \angle 10^\circ} = 30 \angle -30^\circ = \underline{\underline{26 - j15 \Omega}}$




$$\left. \begin{aligned} \frac{-j}{\omega C} &= -j15 \\ \omega &= 2\pi 60 \end{aligned} \right\} C = 177 \mu\text{F}$$

HW Questions

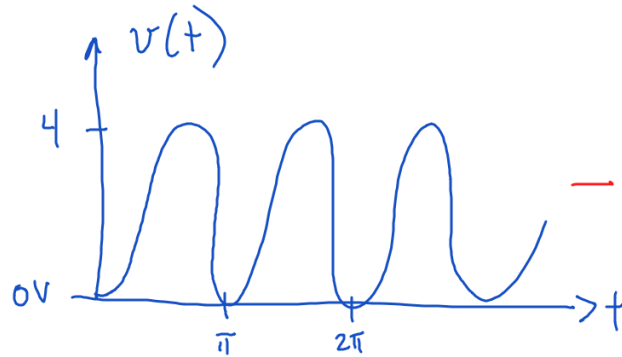

→ V_{rms} guess 2V

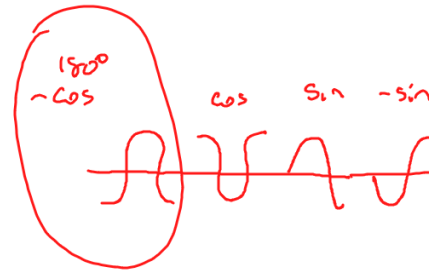

Find V_{rms}

$$v(t) = 2 + 2 \cos(2t + 180^\circ)$$

$$\omega = 2\pi f = 2\pi \frac{1}{\pi} = 2$$

$$f = \frac{1}{\pi}$$

$$T = \pi$$

$$v(t) = 2 + 2 \cos(2t + 180^\circ)$$

$$= 2 - 2 \cos(2t)$$

$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T v^2(t) dt}$$

$$= \sqrt{\frac{1}{\pi} \int_0^\pi (2 - 2 \cos(2t))^2 dt}$$

$$V_{rms}^2 = \frac{1}{\pi} \int_0^\pi 4 - 8 \cos(2t) + 4 \cos^2(2t) dt$$

$$= \frac{1}{\pi} \int_0^{\pi/2} 6 - 8 \cos(2t) + 2 \cos(4t) dt$$

$$= \frac{1}{\pi} 6\pi$$



$$= 6$$

$$V_{rms} = \sqrt{6} = \boxed{2.45 V_{rms}}$$


$$\tan(x + 180^\circ) = -\tan(x)$$

$$\cos(x + 180^\circ) = -\cos(x)$$

$$\sin(x + 180^\circ) = -\sin(x)$$

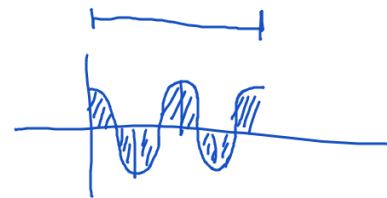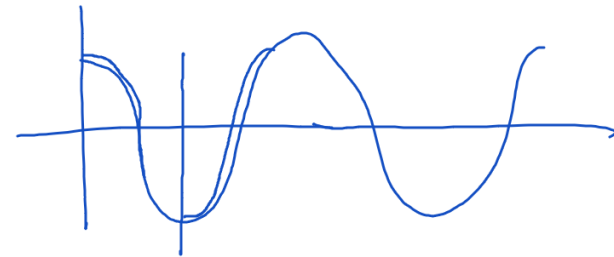

Collaborative Problem

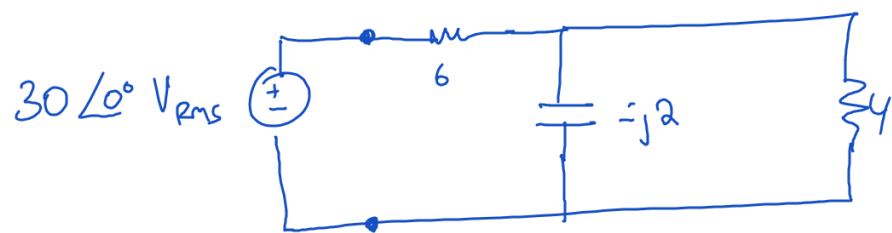

a) Find pf of load as seen by the source. Include whether leading/lagging.

Equivalent circuit diagram for problem a. A voltage source of $30\angle 0^\circ \text{ V}_{\text{rms}}$ is in series with a total impedance of $6 + 4 \parallel -j2$. The total impedance is calculated as $6 + \frac{-j8}{4-j2} = 6.8 - j1.6$.

$$V_{\text{rms}} = 30\angle 0^\circ$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{30\angle 0^\circ}{6.8 - j1.6} = 4.29\angle 13.2^\circ \text{ A}_{\text{rms}}$$

$$\begin{aligned} \text{pf} &= \cos(\theta_I - \theta_V) \\ &= \cos(13.2^\circ - 0^\circ) \\ &= 0.973 \text{ leading} \end{aligned}$$

$$\begin{aligned} \theta_I &> \theta_V \\ 13.2^\circ &> 0^\circ \end{aligned}$$

b) Find S delivered by source. Include units.

$$\begin{aligned} S &= I_{\text{rms}} \cdot V_{\text{rms}} \\ &= (4.29)(30) \\ &= 129 \text{ VA} \end{aligned}$$

c) Find average power P_{ave} delivered by source. Include units.

$$\begin{aligned} P_{\text{ave}} &= S \cdot \text{pf} \\ &= 129 \cdot 0.973 \\ &= 125 \text{ W} \end{aligned}$$

pf: # leading/lagging

S : # VA

P_{ave} : # W