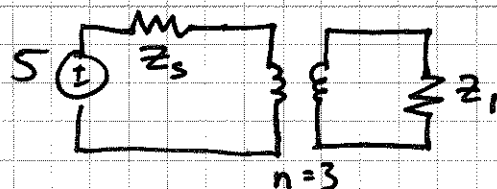


Find R and C to maximize the power dissipated by R


Solution

① C does not dissipate power (C and L never do) so to maximize power dissipated by R we maximize the power dissipated by $\frac{1}{C} \parallel R$. Call that impedance Z_1 .

② Find the Thev equiv to left of transformer, as below



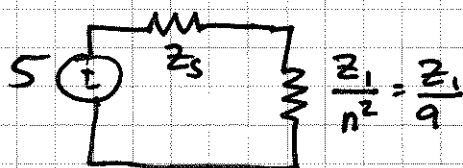③ Plug in Thev equiv to right of transformer



by law of max. power transfer, max power in load occurs when $Z_s = \left(\frac{Z_1}{n^2}\right)^*$

④ Solve Z_s

Z_s , as seen from transformer is: ($Z_C = \frac{1}{j\omega C}$, $Z_L = j\omega L$)

$$Z_s = 5 \parallel \frac{1}{j2(1/5)} + j2.3 = 1 + j4$$

⑤ Solve for Z_1 : $Z_1 = \frac{1}{j2\omega C} + R$

⑥ Apply Law of Max. Power: $Z_s = \left(\frac{Z_1}{n^2}\right)^*$

$$1 + j4 = \left(\frac{1}{j18C} + \frac{R}{9}\right)^* \quad \text{but } \left(\frac{1}{j}\right)^* = (-j)^* = j$$

$$1 + j4 = \frac{j}{18C} + \frac{R}{9} \quad \text{equate real, Imag parts}$$

$$1 = \frac{R}{9} \Rightarrow R = 9 \Omega$$

$$4 = \frac{1}{18C} \Rightarrow C = \frac{1}{72} F$$