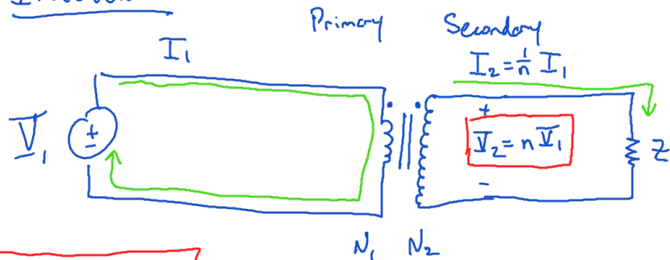


Transformers

- Intuition ✓
- Uses - Impedance Matching ✓
- Power Distribution ✓





Intuition = SSS





Rules for ideal transformer

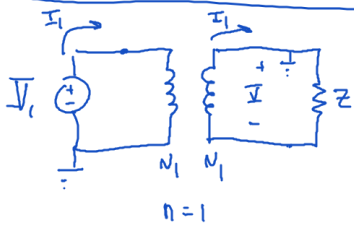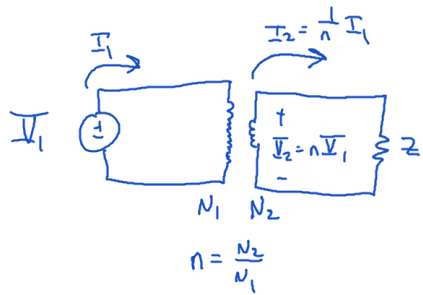
- $V_2 = n V_1$
- $I_2 = \frac{1}{n} I_1$
- only SSS



Thevenin Equivalent = math

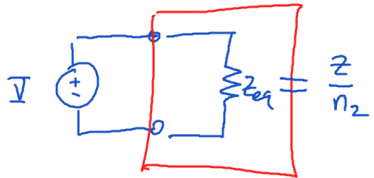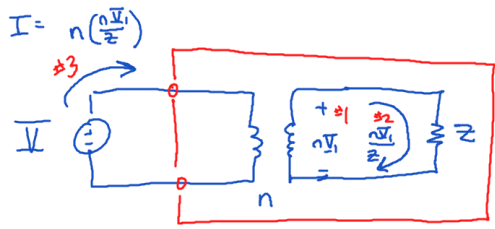

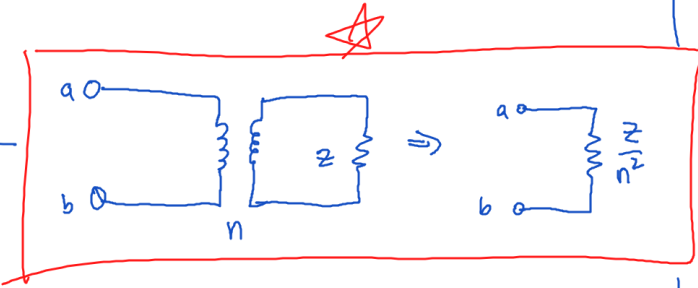
$$Z_{eq} = \frac{V}{I} = \frac{V}{n \left(\frac{n V}{Z} \right)} = \frac{1}{n^2 / Z} = \frac{Z}{n^2}$$




So what? Impedance Matching

Design #1

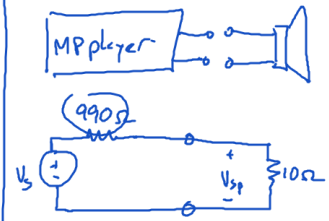

$$P_{sp} = V_{sp} \cdot I_{sp} = \left(V_s \frac{10}{1000} \right) \left(\frac{V_s}{1000} \right) = \frac{V_s^2}{100,000}$$

Design #2

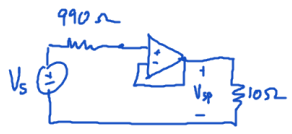



$$P_{sp} = V_{sp} \cdot I_{sp} = (V_s) \cdot \left(\frac{V_s}{10} \right) = \frac{V_s^2}{10}$$

Design #3




$$P_L = I_L \cdot V_L$$

Max Power Transfer Theorem

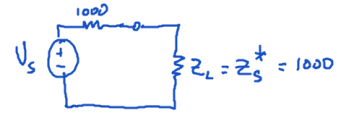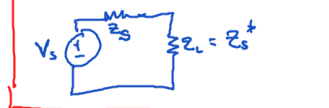

$$\frac{Z_{out}}{n^2} = Z_{desired}$$

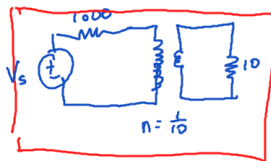
$$\frac{10}{n^2} = 1000 \Rightarrow 10 = 1000 n^2 \Rightarrow n^2 = \frac{10}{1000} \Rightarrow n = \frac{1}{10}$$



$$ex \begin{cases} N_1 = 1000 \\ N_2 = 100 \end{cases}$$


$$P_{sp} = I_{sp} \cdot V_{sp} = \left(\frac{V_s}{2000} \right) \left(\frac{V_s}{2} \right) = \frac{V_s^2}{4000}$$

Power Distribution

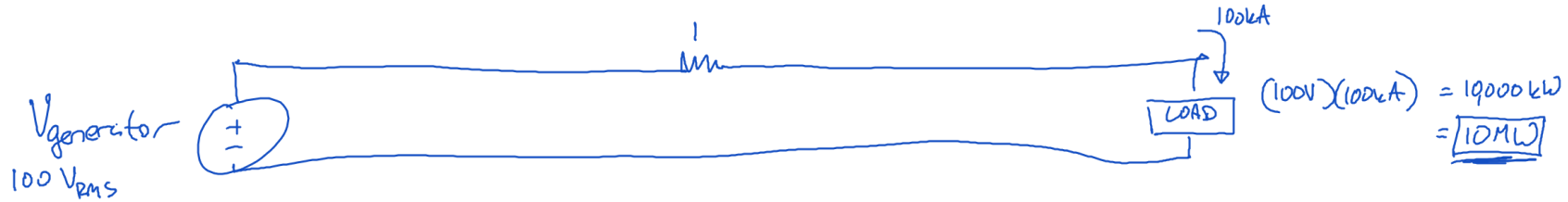

$$\begin{aligned}
 \text{Line loss} &= P_{\text{loss}} \\
 &= I \cdot V_{\text{loss}} \\
 &= I(I \cdot Z_L) \\
 &= I^2 Z \\
 &= (100\text{k})^2 (1) \\
 &= 10000 \text{ M} \\
 &= \boxed{10\text{GW}}
 \end{aligned}$$
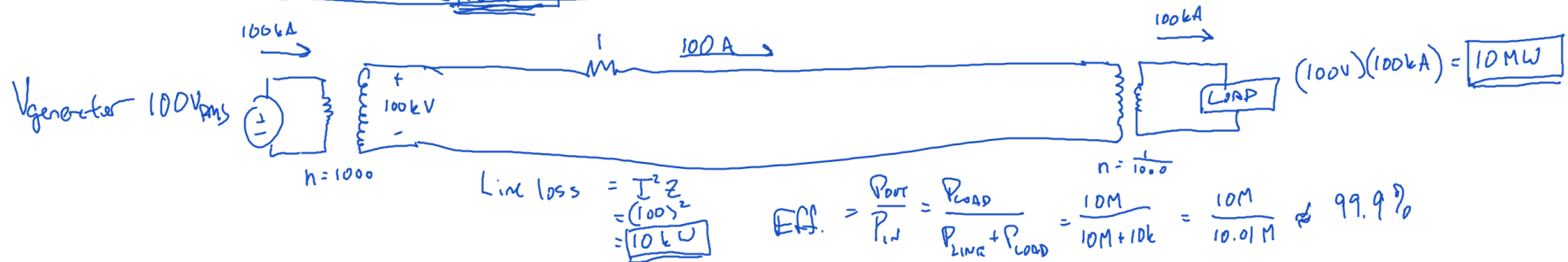
$$\text{Efficiency} = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{LOAD}}}{P_{\text{LINE}} + P_{\text{LOAD}}} = \frac{10\text{M}}{10\text{M} + 10\text{G}} = \frac{10\text{M}}{10.01\text{G}} \approx 0.1\%$$



$$\begin{aligned}
 \text{Line loss} &= I^2 Z \\
 &= (100)^2 \\
 &= \boxed{10\text{kW}}
 \end{aligned}$$

$$\text{Eff.} = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{P_{\text{LOAD}}}{P_{\text{LINE}} + P_{\text{LOAD}}} = \frac{10\text{M}}{10\text{M} + 10\text{k}} = \frac{10\text{M}}{10.01\text{M}} \approx 99.9\%$$