

Since $i(t) = \frac{1}{C} = 0$ for all $t < 0$, C must be initially discharged so $V_c(t=0) = 0$

time Region	t_0	$V(t_0)$	$i(t)$	$V_c(t) = \frac{1}{C} \int_{t_0}^t i(\tau) d\tau + V_c(t_0)$
$t < 0$	—	0 V	0 A	0 V
$0 \leq t \leq 1$	0	0	t^2	$\frac{1}{12} \int_0^t \tau^2 d\tau + 0 = 12 \left(\frac{1}{3} t^3 \right) = 4t^3$
$1 \leq t \leq 2$	1	$4(1)^3 = 4$	1	$12 \int_1^t d\tau + 4 = 12\tau \Big _{\tau=1}^t + 4 = 12t - 12 + 4 = 12t - 8$
$2 \leq t \leq 3$	2	$12(2) - 8 = 16$	$-(t-3) = 3-t$	$12 \int_2^t (3-\tau) d\tau + 16 = 12 \left[3\tau - \frac{1}{2}\tau^2 \right]_{\tau=2}^t + 16 = 12 \left[(3t - \frac{1}{2}t^2) - (6 - 2) \right] + 16 = -6t^2 + 36t - 32$
$t \geq 3$	3	$-6(3)^2 + 36(3) - 32 = 22$	0	$= 12 \int_3^t 0 d\tau + 22 = 22$



a) Find $v_c(t)$

$$V_c(t) = \begin{cases} 0 \text{ V} & , t < 0 \\ 4t^3 \text{ V} & , 0 \leq t < 1 \\ 12t - 8 \text{ V} & , 1 \leq t < 2 \\ -6t^2 + 36t - 32 \text{ V} & , 2 \leq t < 3 \\ 22 \text{ V} & , t \geq 3 \end{cases}$$

b) Find $W_c(2)$


$$W_c(2) = \frac{1}{2} C V_c^2(2) = \frac{1}{2} \left(\frac{1}{12} \right) (16)^2 = \frac{16^2}{24} = 10.7 \text{ J}$$

2)

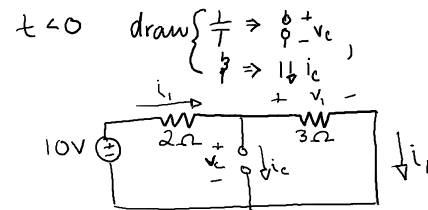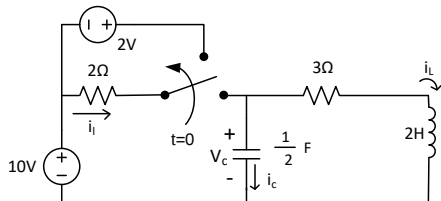

a) Find i_1, i_c, i_L, v_c, v_L , at both $t = -3$ and $t = 0^+$

	$t < 0$ (e.g. $t = -3$)	$t = 0^+$
i_1	$2 \text{ A} \Leftarrow \Omega$'s low	$-1 \text{ A} \Leftarrow \Omega$'s low
i_c	$0 \text{ A} \Leftarrow$ open	$-2 \text{ A} \Leftarrow$ current source
i_L	$2 \text{ A} \Leftarrow \frac{10\text{V}}{5\Omega}$	$2 \text{ A} \Leftarrow$ current continuity $i_L(0^+) = i_L(0^-)$
v_c	$6 \text{ V} \Leftarrow \frac{3}{2+3} 10$	$6 \text{ V} \Leftarrow$ voltage continuity $V_c(0^+) = V_c(0^-)$
v_L	$0 \text{ V} \Leftarrow$ short	$0 \text{ V} \Leftarrow \text{KVL} + 3(2) + V_c - 6 = 0$

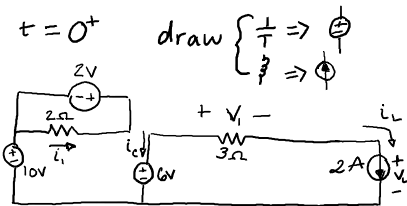


b) Find $Q_c(t = -2)$, $W_L(t = 0^+)$


$$Q(t = -2) = C V_c(t = -2) = \left(\frac{1}{2} F\right)(6V) = \boxed{3C}$$

$$W_L(t = 0^+) = \frac{1}{2} L i_L^2(0^+) = \frac{1}{2} (2)(2)^2 = \boxed{4J}$$

3) Find $v(t)$ and $i(t)$ for all time

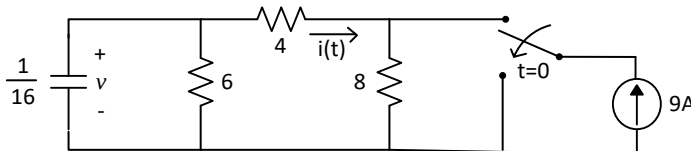

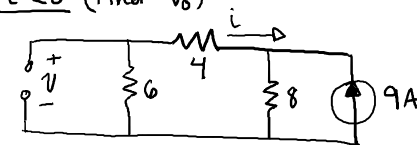to find $V(t)$ must first find V_0 , V_{∞} , τ . To find $i(t)$, note $i(t) = \frac{V(t)}{4+8}$
 $t < 0$ (find V_0)




by i divider, $i = -\frac{8}{8+10} \cdot 9 = \boxed{-4A}$
 by Ω 's law, $V_0 = -6i = \boxed{24V}$

$t = \infty$ (find V_{∞})



$V_{\infty} = 0$
 by inspection
 (no source)

$t > 0$ (find τ)

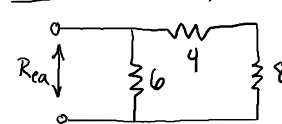


$$R_{eq} = 6 // 12 = 4\Omega$$

$$\tau = R_{eq} C = \left(\frac{1}{16}\right) 4 = \boxed{\frac{1}{4} \text{ sec}}$$

$$V(t) = \begin{cases} 24V, & t < 0 \\ V_{\infty} + (V_0 - V_{\infty}) e^{-t/\tau}, & t > 0 \end{cases} = \begin{cases} 24V, & t < 0 \\ 24e^{-4t}, & t > 0 \end{cases}$$

$$i(t) = \begin{cases} -4A, & t < 0 \\ \frac{V_c}{4+8}, & t > 0 \end{cases} = \begin{cases} -4A, & t < 0 \\ 2e^{-4t} A, & t > 0 \end{cases}$$

4) Find $v_L(t)$, $t \geq 0$

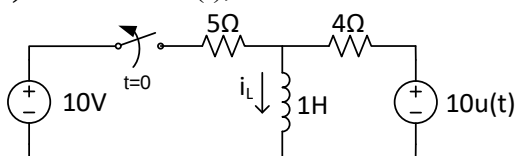


$t < 0$

$$I_0 = \frac{10V}{5\Omega} = \boxed{2A}$$




$t > 0$

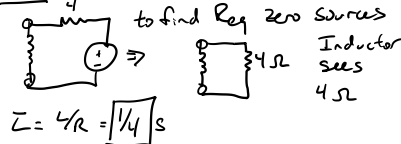

$$\tau = L/R = \boxed{1/4 \text{ s}}$$

$t = \infty$

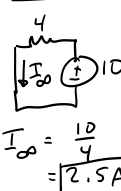


$$I_{\infty} = \frac{10}{4} = \boxed{2.5A}$$


$$i_L(t) = I_{\infty} + (I_0 - I_{\infty}) e^{-t/\tau} = 2.5 + (2 - 2.5) e^{-4t} = \boxed{2.5 - 0.5e^{-4t}}$$

$$v_L = L i_L' = (1H) \frac{d}{dt} (2.5 - 0.5e^{-4t}) = 0 - 0.5(-4)e^{-4t} = \boxed{2e^{-4t} V}$$

5) Find $v_o(t)$, $t \geq 0$

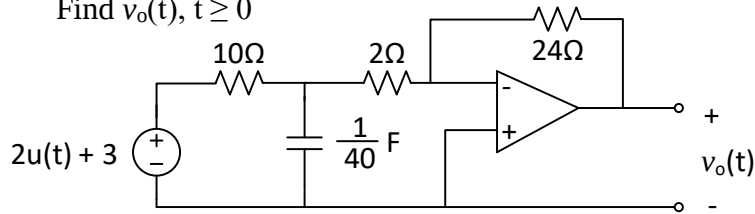


$t < 0$

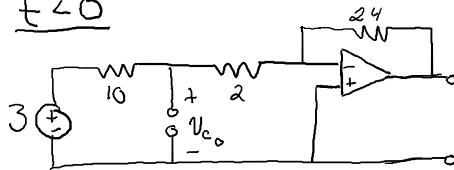

$$\text{KCL @ } v_c: \frac{v_c - 3}{10} + \frac{v_c - 0}{2} = 0$$


$$v_c(0) = \frac{1}{2}$$

$t = \infty$

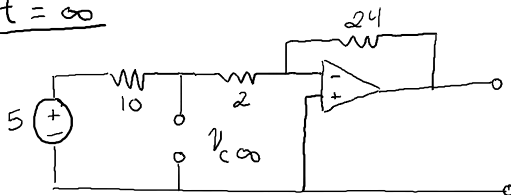

$$\text{KCL @ } v_c: \frac{v_c - 5}{10} + \frac{v_c - 0}{2} \Rightarrow v_{\infty} = \frac{5}{6}$$

τ

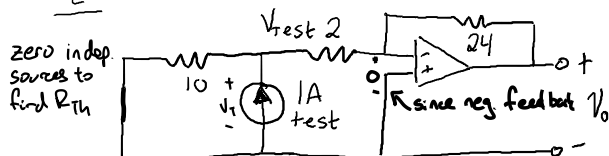


$$\text{KCL above } 1A: \frac{v_{\text{test}}}{10} - 1 + \frac{v_{\text{test}} - 0}{2} = 0$$

$$\text{Solve for } v_{\text{test}} = \frac{5}{3} \Rightarrow R_{\text{eq}} = \frac{v_{\text{test}}}{I_{\text{test}}} = \frac{5}{3}$$

$$\tau = R_{\text{eq}} \cdot C = \frac{5}{3} \cdot \frac{1}{40} = \frac{1}{24}$$
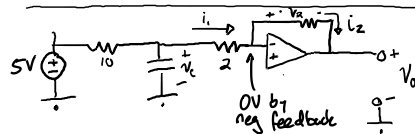
$$v_c(t) = v_{\infty} + (v_0 - v_{\infty})e^{-t/\tau} = \left[\frac{5}{6} - \frac{1}{3}e^{-24t} \right] \text{ BUT we want } v_o, \text{ not } v_c$$



To find v_o given v_c , ① $i_1 = \frac{v_c - 0}{2}$

$$\text{② } i_2 = i_1 = \frac{v_c}{2}$$

$$\text{③ } v_R = 24 \cdot i_2 = 24 \left(\frac{v_c}{2} \right) = 12v_c$$

$$\text{④ } v_o = 0 - v_R = -12v_c = -12 \left(\frac{5}{6} - \frac{1}{3}e^{-24t} \right) = \boxed{-10 + 4e^{-24t} \text{ V}}$$