
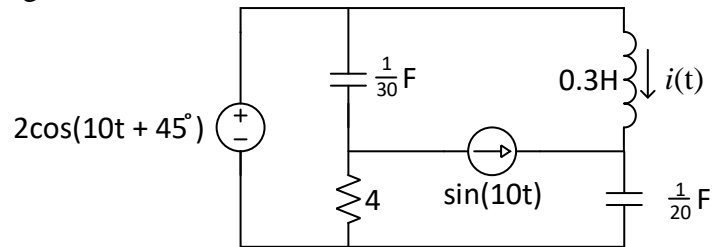


1. Find  $i(t)$  using mesh

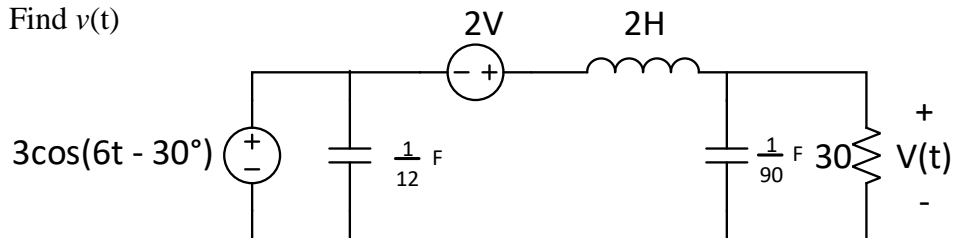

2. Find  $v(t)$



3. Find Thevenin equivalent in the time-domain (i.e. with an impedance made of a resistor in series with a capacitor or inductor)

