
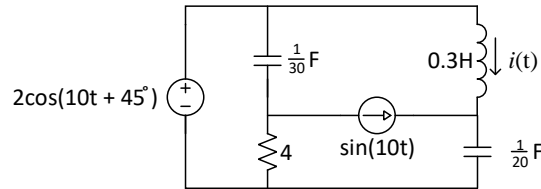


1. Find  $i(t)$  using mesh

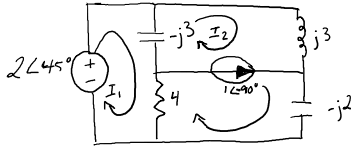

Method 1: brute-force Mesh Current Analysis. Three meshes, so 3x3 set of equations.

$$\text{KVL } I_1: -2\angle 45^\circ + (I_1 - I_2)(-j3) + (I_1 - I_3)4 = 0 \Rightarrow I_1(4 - j3) + I_2(j3) + I_3(-4) = 2\angle 45^\circ$$

$$\text{KVL Supermesh (right mesh)}: I_2(j3) + I_3(-j2) + (I_3 - I_1)4 + (I_2 - I_1)(-j3) = 0$$


$$\Rightarrow I_1(-4 + j3) + I_2(j3 - j3) + I_3(4 - j2) = 0 \Rightarrow I_1(-4 + j3) + I_3(4 - j2) = 0$$

$$\text{Extra eqn for Supermesh: } I_3 - I_2 = 1\angle -90^\circ \Rightarrow I_2(-1) + I_3 = 1\angle -90^\circ$$

$$\begin{bmatrix} 4-j3 & j3 & -4 \\ -4+j3 & 0 & 4-j2 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 2\angle 45^\circ \\ 0 \\ 1\angle -90^\circ \end{bmatrix} \Rightarrow \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 4.15 \angle -61.9^\circ \\ 3.70 \angle -67.5^\circ \\ 4.63 \angle -72.2^\circ \end{bmatrix} \Rightarrow \boxed{i_2(t) = 3.70 \cos(10t - 67.5^\circ) \text{ A}}$$

Smart tip: recognize  $1\angle -90^\circ = -j$  which is easier to put into the calculator

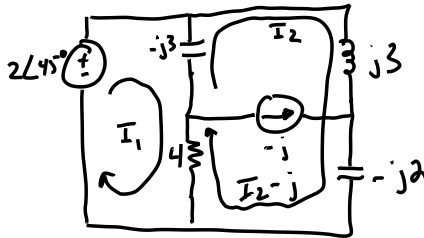Method 2: Smarter: recognize we could do it with just 2 meshes;  $I_1$  and a supermesh around the whole right side named  $I_2$  and  $I_2$  + the current source



$$\text{KVL } I_1: -2\angle 45^\circ + (I_1 - I_2)(-j3) + (I_1 - (I_2 - j))4 = 0$$

$$\Rightarrow I_1(4 - j3) + I_2(-4 + j3) = 2\angle 45^\circ - j4$$

$$\text{KVL right side: } -j3(I_2 - I_1) + j3I_2 - j2(I_2 - j) + 4(I_2 - j - I_1) = 0$$

$$\Rightarrow I_1(-4 + j3) + I_2(-j3 + j3 - j2 + 4) + j^2 2 - j4 = 0$$


$$= I_1(-4 + j3) + I_2(4 - j2) = 2 + j4$$

$$\begin{bmatrix} 4-j3 & -4+j3 \\ -4+j3 & 4-j2 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2\angle 45^\circ - j4 \\ 2 + j4 \end{bmatrix}$$

$$\Rightarrow I_2 = 3.70\angle -67.5^\circ$$

$$\Rightarrow \boxed{i_2(t) = 3.70 \cos(10t - 67.5^\circ) \text{ A}}$$

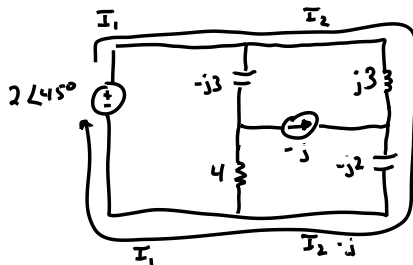Method 3: Smartest: recognize that just one supermesh around the outside would solve the whole thing for  $I_2$ .



$$\text{KVL outside: } -2\angle 45^\circ + j3I_2 - j2(I_2 - j) = 0$$


$$\Rightarrow I_2(j3 - j2) - 2\angle 45^\circ + j^2 2 = 0$$

$$\Rightarrow I_2 j = 2\angle 45^\circ + 2$$

$$\Rightarrow I_2 = \frac{2 + 2\angle 45^\circ}{j} = 3.70\angle -67.5^\circ$$


$$\Rightarrow \boxed{i_2(t) = 3.70 \cos(10t - 67.5^\circ) \text{ A}}$$

2. Find  $v(t)$

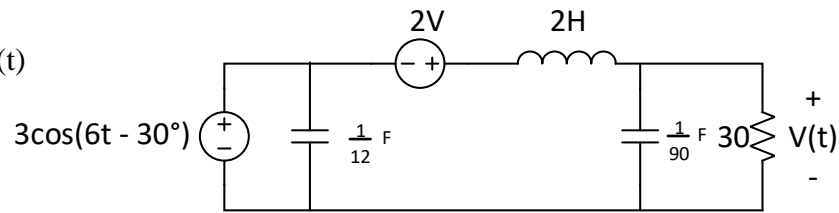


2 different frequencies,  $\omega=6$  and  $\omega=0$ , so must use Superposition

① Left V

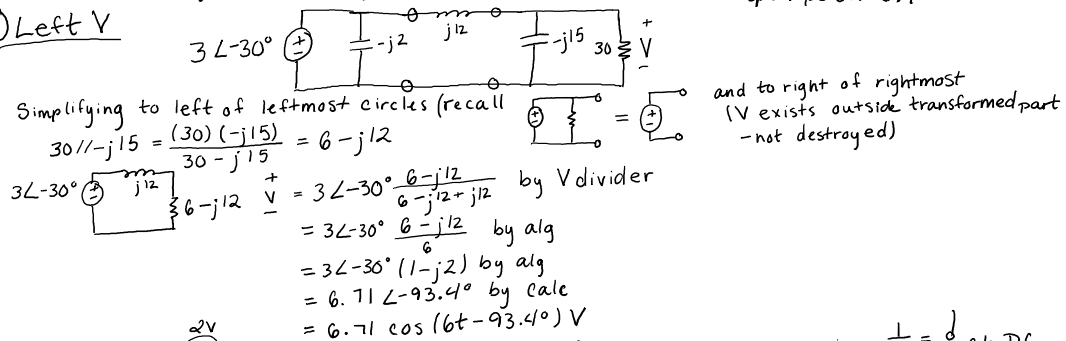


② Top V

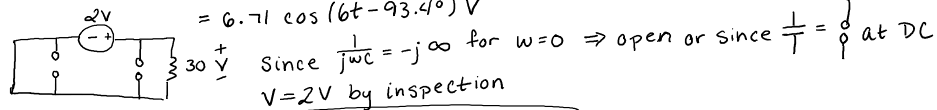


$$V(t) = 6.71 \cos(6t - 93.4^\circ) + 2\text{V}$$

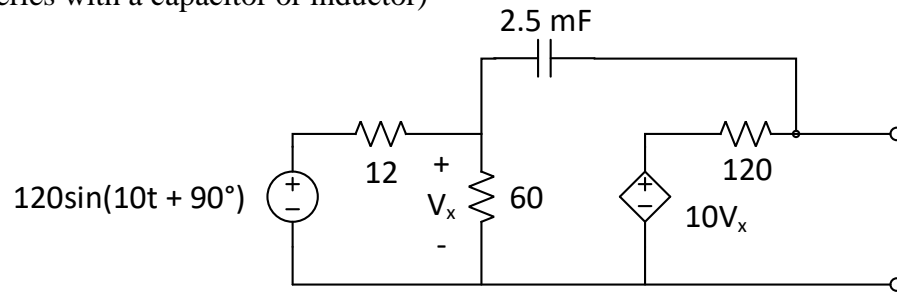3. Find Thevenin equivalent in the time-domain (i.e. with an impedance made of a resistor in series with a capacitor or inductor)



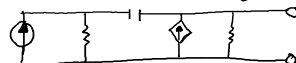Plan: ① Can we do some transforms + Simplification?




no, not all the way or we will lose  $V_x$

② Can we find  $V_{oc}$  then zero all sources to find  $Z_{eq}$ ?

no, because of dependent source

③ Find  $V_{oc}$ , then  $I_{sc}$ , then divide to find  $Z_{eq}$

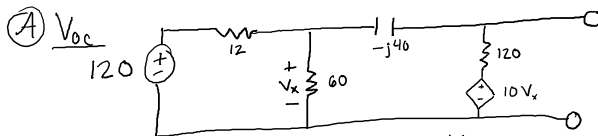(If all sources were dependent, we would have to use a test source!)




Mesh  $\Rightarrow$  3 unknown meshes

Nodal  $\Rightarrow$  2 unknown nodes  $\star$

$$\text{KCL @ } V_x: \frac{V_x - 120}{12} + \frac{V_x}{60} + \frac{V_x - V_{oc}}{-j40} = 0 \Rightarrow V_x \left[ \frac{1}{12} + \frac{1}{60} + \frac{1}{-j40} \right] + V_{oc} \left( \frac{1}{j40} \right) = 10$$

$$\text{KCL @ } V_{oc}: \frac{V_{oc} - V_x}{-j40} + \frac{V_{oc} - 10V_x}{120} = 0 \Rightarrow V_x \left[ \frac{1}{-j40} - \frac{1}{12} \right] + V_{oc} \left[ \frac{1}{-j40} + \frac{1}{120} \right] = 0$$

$$\begin{bmatrix} \frac{1}{12} + \frac{1}{60} - \frac{1}{j40} & \frac{1}{j40} \\ \frac{1}{-j40} - \frac{1}{12} & \frac{1}{-j40} + \frac{1}{120} \end{bmatrix} \begin{bmatrix} V_x \\ V_{oc} \end{bmatrix} = \begin{bmatrix} 10 \\ 0 \end{bmatrix} \Rightarrow \begin{bmatrix} V_x \\ V_{oc} \end{bmatrix} = \begin{bmatrix} 253 \angle 34.7^\circ \\ 835 \angle -20.2^\circ \end{bmatrix} \quad \boxed{V_{oc} = 835 \angle -20.2^\circ \text{ V}}$$

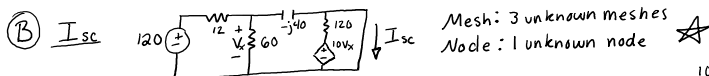

Mesh: 3 unknown meshes

Node: 1 unknown node  $\star$

$$\text{KCL @ } V_x: \frac{V_x - 120}{12} + \frac{V_x}{60} + \frac{V_x}{-j40} = 0 \Rightarrow V_x \left( \frac{1}{12} + \frac{1}{60} + \frac{1}{-j40} \right) = \frac{120}{12} \Rightarrow V_x = \frac{10}{\frac{1}{12} + \frac{1}{60} + \frac{1}{-j40}} \quad \text{since } \frac{1}{-j} = j = 97 \angle -14^\circ \text{ V}$$

To find  $I_{sc}$  now that  $V_x$  is known, many ways. One is:

$$\begin{aligned} \text{KCL upper-right: } I_{sc} + \frac{0 - 10V_x}{120} + \frac{0 - V_x}{-j40} &= 0 \\ I_{sc} &= V_x \left( \frac{10}{120} + \frac{1}{j40} \right) \quad \text{since } \frac{1}{j} = -j(10) = 2.6 \text{ mF} \\ &= (97 \angle -14^\circ) \left( \frac{1}{12} + \frac{1}{-j40} \right) \\ I_{sc} &= 8.44 \angle 2.66^\circ \text{ A} \end{aligned}$$

③  $Z_{eq} = \frac{V_{oc}}{I_{sc}} = \frac{835 \angle -20.2^\circ}{8.44 \angle 2.66^\circ} = 91.2 - j38.4$

$$Z_c = -j38.4 = \frac{1}{j\omega C} = \frac{-j}{10C} \Rightarrow j = (-j38.4)(10C) \Rightarrow C = \frac{1}{384}$$

