

**Concept:** Impulse Response

**Find:** Find the impulse response (the circuit's response to an impulse input) of the circuit.

**Hint:** The solution has both a step and impulse

