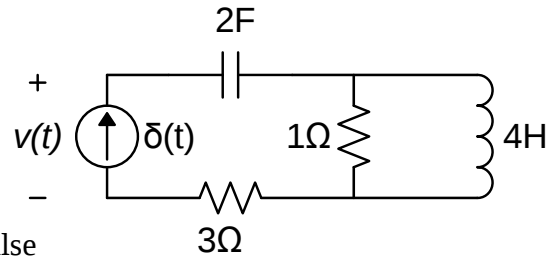



Concept: Impulse Response

Find: Find the impulse response (the circuit's response to an impulse input) of the circuit.


Hint: The solution has both a step and impulse



Freq Domain

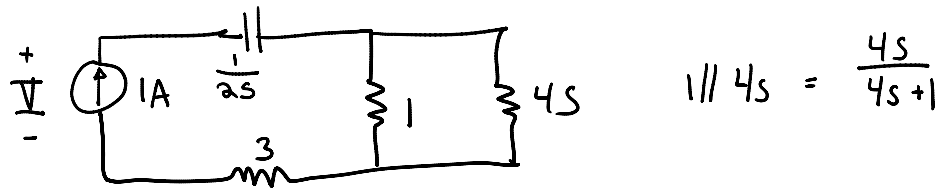

$$1 \parallel 4s = \frac{4s}{4s+1}$$

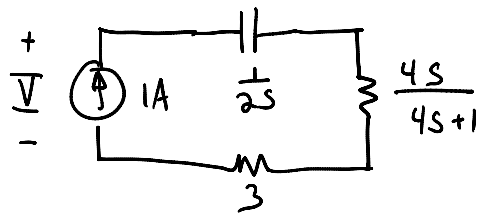

$$\underline{V} = \underline{I} \cdot \underline{Z}$$

$$= 1 \left(\frac{1}{2s} + \frac{4s}{4s+1} + 3 \right)$$

Don't put over common den -
you just have to split it out
to find inverse transform!

$$= \frac{1}{2s} + \frac{s}{s+1/4} + 3$$

improper $\rightarrow s+1/4 \left[\frac{s}{s+1/4} - \frac{1/4}{s+1/4} \right]$

$$= \frac{1}{2s} + \left(1 - \frac{1/4}{s+1/4} \right) + 3$$

$$= \frac{1}{2s} - \frac{1/4}{s+1/4} + 4 \quad \text{Now reap the benefits of not putting over a common den}$$

$$\Leftrightarrow \left[\frac{1}{2} - \frac{1}{4} e^{-\frac{1}{4}t} \right] u(t) + 4 \delta(t)$$