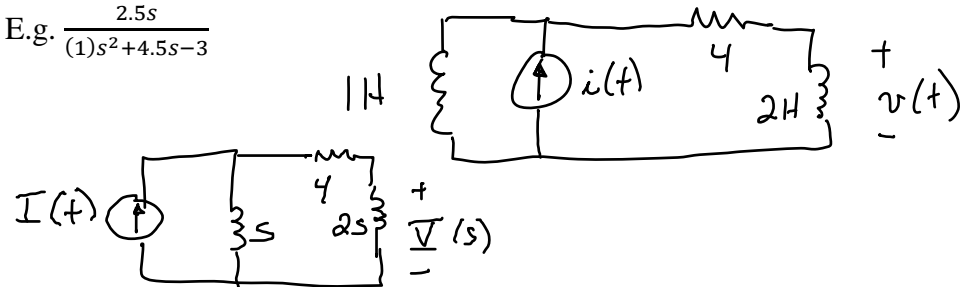


CP 1

Find $H(s) = \frac{V(s)}{I(s)}$ of the circuit below. Write it as a ratio of polynomials in standard form. That means, in the denominator, the coefficient of s of the highest power is 1.

E.g. $\frac{2.5s}{(1)s^2 + 4.5s - 3}$



$$sI(s) \cdot \left(\frac{4}{s} \right) = I(s) \cdot s \cdot \frac{2s}{3s+4} \text{ by } V_{\text{divider}}$$

$$\frac{V(s)}{I(s)} = \frac{2s^2}{3s+4} = \boxed{\frac{\frac{2}{3}s^2}{s + \frac{4}{3}}}$$

CP 2

Find the impulse response of the above circuit

Improper fraction: $s + \frac{4}{3} \overline{\frac{\frac{2}{3}s^2 - \frac{4}{9}}{\frac{2}{3}s^2 + \frac{4}{9}s}}$

$$H(s) = s + \frac{4}{3} + \frac{\frac{16}{27}}{s + \frac{4}{3}}$$

$$h(t) = \delta'(t) + \frac{4}{3}\delta(t) + \frac{16}{27}e^{-\frac{4}{3}t}u(t)$$