

P1 Concept: Equivalent system representations

Find: Given the circuit with

input $v_s(t)$, output $i(t)$ find:


a) system transfer function $H(s)$

b) s-plane plot

c) differential equation

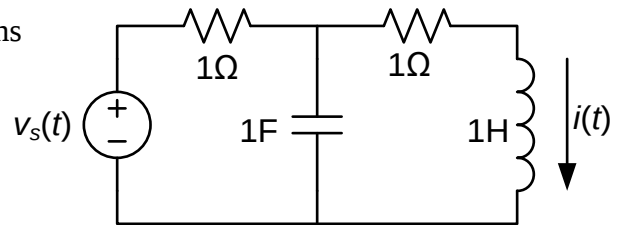d) impulse response $h(t)$

Hint: Its impulse response oscillates with a frequency of $\omega = 1$ rad/sec



First, consider approach. Mesh (2 unknowns) beats nodal (2 unknowns) because result in terms of I . But even easier is to first use source transforms / Z simplification


by I divider

$$I = V_s \left(\frac{\frac{1}{s+1}}{\frac{1}{s+1} + s+1} \right) = V_s \left(\frac{1}{1 + (s+1)^2} \right)$$

$$H(s) = \frac{I(s)}{V_s(s)} = \frac{1}{(s+1)^2 + 1}$$

$$H(s) = \frac{1}{s^2 + 2s + 2}$$

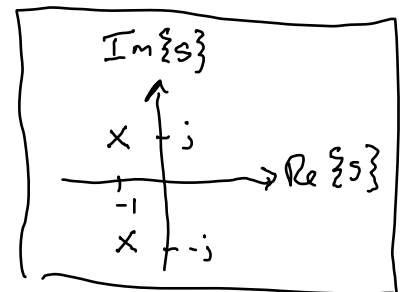b) no zeros, poles: $s = \frac{-2 \pm \sqrt{4-8}}{2} = -1 \pm j$



c) $\frac{I(s)}{V_s(s)} = \frac{1}{s^2 + 2s + 2}$ cross mult

$$I(s)[s^2 + 2s + 2] = V_s(s)$$

$$\ddot{i} + 2\dot{i} + 2i = v_s$$

d) could multiply out, find complex roots, etc., but simpler to see $\frac{1}{(s+1)^2 + 1}$ in table has the transform

$$h(t) = e^{-t} \sin(t) u(t)$$