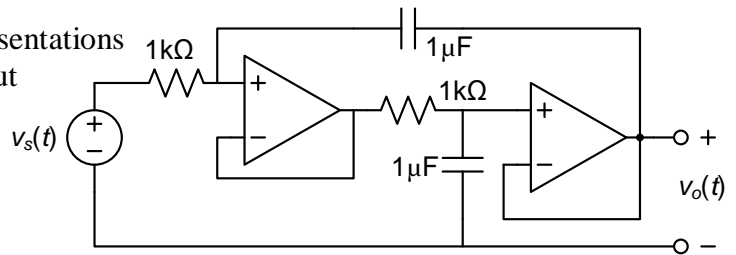


P1 Concept: Equivalent system representations

Find: Given the circuit with input

$v_s(t)$, output $v_o(t)$ find:

- transfer function $H(s)$
- s-plane plot
- differential equation
- impulse response $h(t)$



Hints: • It's easier to manipulate C/s than 1000000/s

• The only digits in $H(s)$ are 1, 10^3 , and 10^6

Note: This is not “just” a homework problem, but a very real-world lowpass filter

P2 Concept: S-Plane representation

Find: Which of the below s-plane system representations are

- Unstable?
- Have impulse responses that oscillate?
- Which could have an impulse response of $h(t) = u(t)$?
- Two of the impulse responses are $h_1(t) = e^{-t}u(t)$ and $h_2(t) = e^{-3t}u(t)$. Which s-plane plot corresponds to h_1 ?

Hint: Find the corresponding $H(s)$ for each s-plane first

