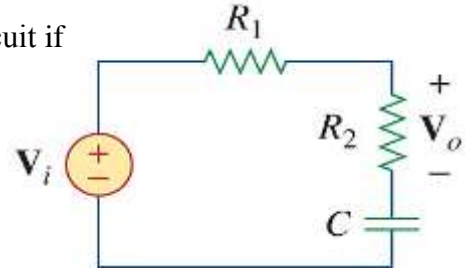


**Find:** The transfer function  $H(\omega)$  for the following circuit if  $R_1 = 10\Omega$ ,  $R_2 = 2\Omega$ , and  $C = 1/8F$ .

Voltage divider

$$V_o = \frac{2}{10+2+\frac{8}{s}} V_i \Rightarrow H(s) = \frac{V_o}{V_i} = \frac{2s}{12s+8}$$

$$H(\omega) = \frac{j2\omega}{12j\omega+8}$$



**Find:**  $v_o(t)$  of the above circuit if  $v_i(t) = \cos(10t)$ . You'll need a calculator.

$$H(10) = \frac{j2 \cdot 10}{12 \cdot 10j + 8} = 0.166 \angle 3.8^\circ$$

$$v_o(t) = 0.166 \cos(10t + 3.8^\circ) V$$