


P1 Concept: Deriving transfer function $H(\omega)$ and its use in SSS analysis

Find: a) $H(\omega)$ of the circuit if $L = 2\text{H}$, $R = 20\Omega$, and $C = 0.1\text{F}$ and

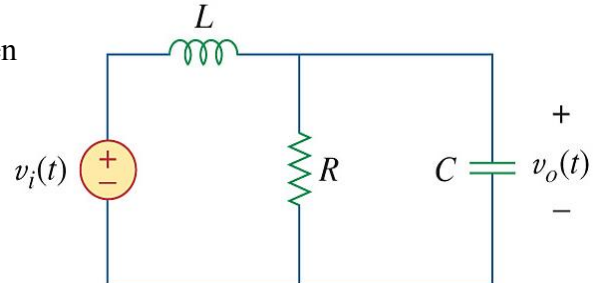b) find $v_o(t)$ if $v_i(t) = \cos(2t)$

Hints:

- There are 5's in the num and den
- $H(\omega)$ is a function of ω , not s !
- The phase angle of v_o is "nice"



P2 Concept: Deriving transfer function $H(\omega)$ and its use in SSS analysis

Find: a) $H(\omega)$ of the circuit. Write as a simple polynomial ratio.

b) tell if it is a lowpass (passes low frequencies, blocks high ones) or highpass filter (passes high freqs, blocks low ones).

Hints:

- Try substituting $\omega = 0$ and ∞ to see if the filter is a low or highpass.
- The numerator is $j\omega RL$, where R is either R_1 or R_2 .

