



Given: The above periodic input to the above circuit fragment

Find: An approximation to $v_o(t)$ consisting of the DC and first two harmonics.
Coefficients should be numeric, not functional (e.g. 1.27 not $4/\pi$).