

Objectives

- Instantaneous Power
- Average Power
- Parseval's Theorem
 - Example of Parseval's
- Real-World Example

Instantaneous Power

$$p(t) = i(t) \cdot v(t) \quad \text{any waveform, periodic or not}$$

Average Power (only periodic)


$$P = \frac{1}{T} \int_{\langle T \rangle} p(t) dt \quad \text{any periodic waveform}$$

$$= \frac{1}{2} V_m I_m \cos(\theta_v - \theta_i) \quad \text{for SSS} = \begin{cases} v(t) = V_m \cos(\omega t + \theta_v) \\ i(t) = I_m \cos(\omega t + \theta_i) \end{cases}$$

$$= V_{DC} \cdot I_{DC} + \frac{1}{2} \sum_{n=1}^{\infty} V_n I_n \cos(\phi_{vn} - \phi_{in})$$

$$\text{for any periodic} \begin{cases} v(t) = V_{DC} + \sum_{n=1}^{\infty} V_n \cos(n\omega_0 t + \phi_{vn}) \\ i(t) = I_{DC} + \sum_{n=1}^{\infty} I_n \cos(n\omega_0 t + \phi_{in}) \end{cases}$$
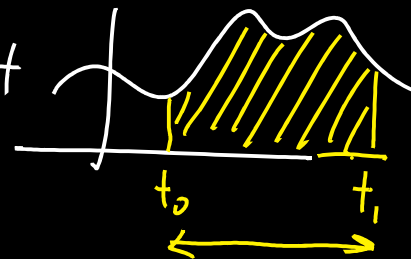
$$P = \frac{1}{t_1 - t_0} \int_{t_0}^{t_1} p(t) dt$$



$$\text{Power in a harmonic} \begin{cases} A_0^2 & \text{if } n=0 \\ \frac{1}{2} A_n^2 & \text{if } n>0 \end{cases} \quad \begin{array}{l} \text{(if a voltage is applied to} \\ \text{a } 1 \Omega \text{ resistor)} \end{array}$$


Parseval's Theorem

Average power P of periodic signal $v(t)$ = DC average power + AC average powers

$$P = V_{\text{rms}}^2 = \frac{1}{T} \int_{\langle T \rangle} v^2(t) dt = \begin{cases} A_0^2 + \frac{1}{2} \sum_{n=1}^{\infty} A_n^2 \\ a_0^2 + \frac{1}{2} \sum_{n=1}^{\infty} (a_n^2 + b_n^2) \end{cases}$$

So? ① Lets you compute V_{rms} quickly given FS
② " " determine what % total power is at a specific frequency

Parseval's Example

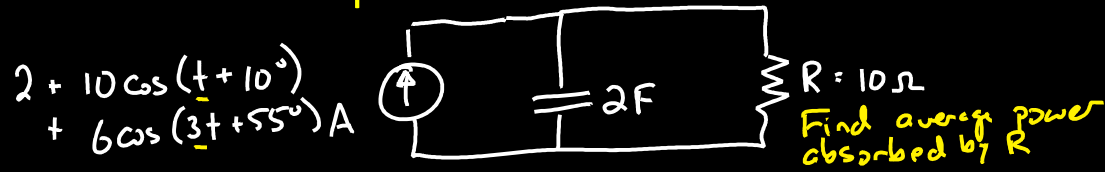

$$P_{\text{ave}} = P_{\text{DC}} + P_{\text{freq1}} + P_{\text{freq2}} + \dots$$

$$= \underline{V_{\text{DC}}} \underline{I_{\text{DC}}} + \frac{1}{2} \sum_{n=1}^{\infty} (V_n \cdot I_n) \cos(\phi_{Vn} - \phi_{In})$$

① DC

$$\left. \begin{array}{l} V_{\text{DC}} = 20 \text{ V} \\ I_{\text{DC}} = 2 \text{ A} \end{array} \right\} P_{\text{DC}} = 40 \text{ W}$$

② $\omega = 1$

$$\left. \begin{array}{l} V_1 = (10 \angle 10^\circ) \left(\frac{-j10}{20 - j} \right) = 5 \angle -77.1^\circ \\ I_1 = \frac{5 \angle -77.1^\circ}{10} = 0.5 \angle -77.1^\circ \end{array} \right\} P_1 = \frac{1}{2} (5)(0.5) \cos(0^\circ) = 1.25 \text{ W}$$

③ $\omega = 3$

$$\left. \begin{array}{l} V_3 = (6 \angle 55^\circ) \left(\frac{1}{j6} \parallel 10 \right) = 1 \angle -54^\circ \\ I_3 = V_3 / 10 = 0.1 \angle -54^\circ \end{array} \right\} P_3 = \frac{1}{2} (1)(0.1) \cos(0) = 0.05$$

$$P_{\text{ave}} = 40 + 1.25 + 0.05 = 41.3 \text{ W}$$

$$P = \frac{V_{\text{rms}}^2}{R} = \frac{1}{T} \int_{\langle T \rangle} v^2(t) dt = \left(A_0^2 + \frac{1}{2} \sum_{n=1}^{\infty} A_n^2 \right) = \left(a_0^2 + \frac{1}{2} \sum_{n=1}^{\infty} (a_n^2 + b_n^2) \right)$$

$$\frac{1}{j \cdot 1 \cdot 2} = \frac{1}{j2} = -j \frac{1}{2}$$

$$\frac{1}{j} \cdot \frac{j}{2} = \frac{j}{j2} = \frac{j}{-1} = -j$$

$$Z = \left(-\frac{j}{2} \right) \parallel 10 = \frac{-j5}{10 - j/2} = \frac{-j10}{20 - j}$$

Parseval's Example 2

$$v(t) = 3 + 2\cos(2t) - \cos(4t - 20^\circ) \quad \text{Find } V_{\text{RMS}}$$

Method 1: $V_{\text{RMS}} = \sqrt{\frac{1}{T} \int_{\langle T \rangle} v^2(t) dt}$ Painful!

Method 2: $P = I_{\text{RMS}}^2 = A_0^2 + \frac{1}{2} \sum_{n=1}^{\infty} A_n^2$



$$= 3^2 + \frac{1}{2}(2^2 + (-1)^2)$$

$$= 9 + \frac{1}{2}(5)$$

$$= 11.5$$

$$V_{\text{RMS}} = \sqrt{11.5} = \boxed{3.39 \text{ V}_{\text{RMS}}}$$

Real World Example

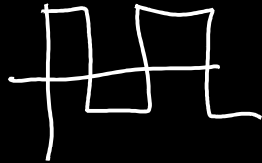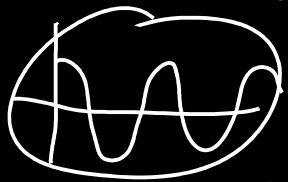

99% spectrally pure

$$\text{Test} = \frac{\text{Power } 60 \text{ Hz}}{\text{Total Power}} \geq 0.99$$

$$\frac{\frac{1}{2} A_1^2}{V_{\text{RMS}}^2} \geq 0.99$$