

All questions refer to a power generator producing a voltage of

$$v(t) = 30 + 20 \cos(60\pi t + 45^\circ) + 10 \cos(120\pi t + 45^\circ) \text{ V}$$

with an exiting current of

$$i(t) = 6 + 4 \cos(60\pi t + 10^\circ) + 2 \cos(120\pi t + 120^\circ) \text{ A}$$

**Find:** The  $V_{\text{RMS}}$  of the voltage waveform

**Find:** The  $I_{\text{RMS}}$  of the voltage waveform

**Find:** The total average power delivered by the generator

**Find:** (Real-world) The device is supposed to deliver a pure DC source but it appears to have some contamination from nearby electronic devices. What is the percentage of the total output power contaminated by 60Hz?