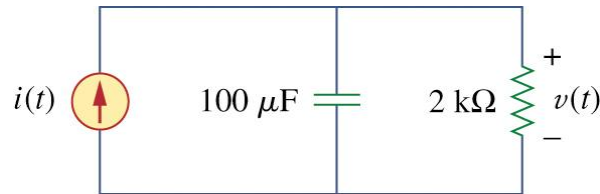


In the circuit below, $i(t) = 20 + 16 \cos(10t + 45^\circ) + 12 \cos(20t - 60^\circ)$ mA



- P1 Concept:** Frequency response
Find: $v(t)$
Hint: One part of the answer is $14.3 \cos(10t - 18.4^\circ)$
- P2 Concept:** Average power given sum of sinusoids
Find: The average power dissipated by the resistor
Hint: Answer is between 800mW and 900mW
- P3 Concept:** RMS values of a sum of sinusoids
Find: I_{RMS} (not V_{RMS})
Hint: Answer is between 10mA_{RMS} and 30mA_{RMS}
- P4 Concept:** Power delivered to a normalized load at a specific frequency
Find: Power delivered by the $5/\pi$ Hz component of the source if attached to a 1Ω load.
Hints: You can find it directly from one of the $A\angle\theta$ components of the source.
The answer is between 100 and $200\mu\text{W}$.