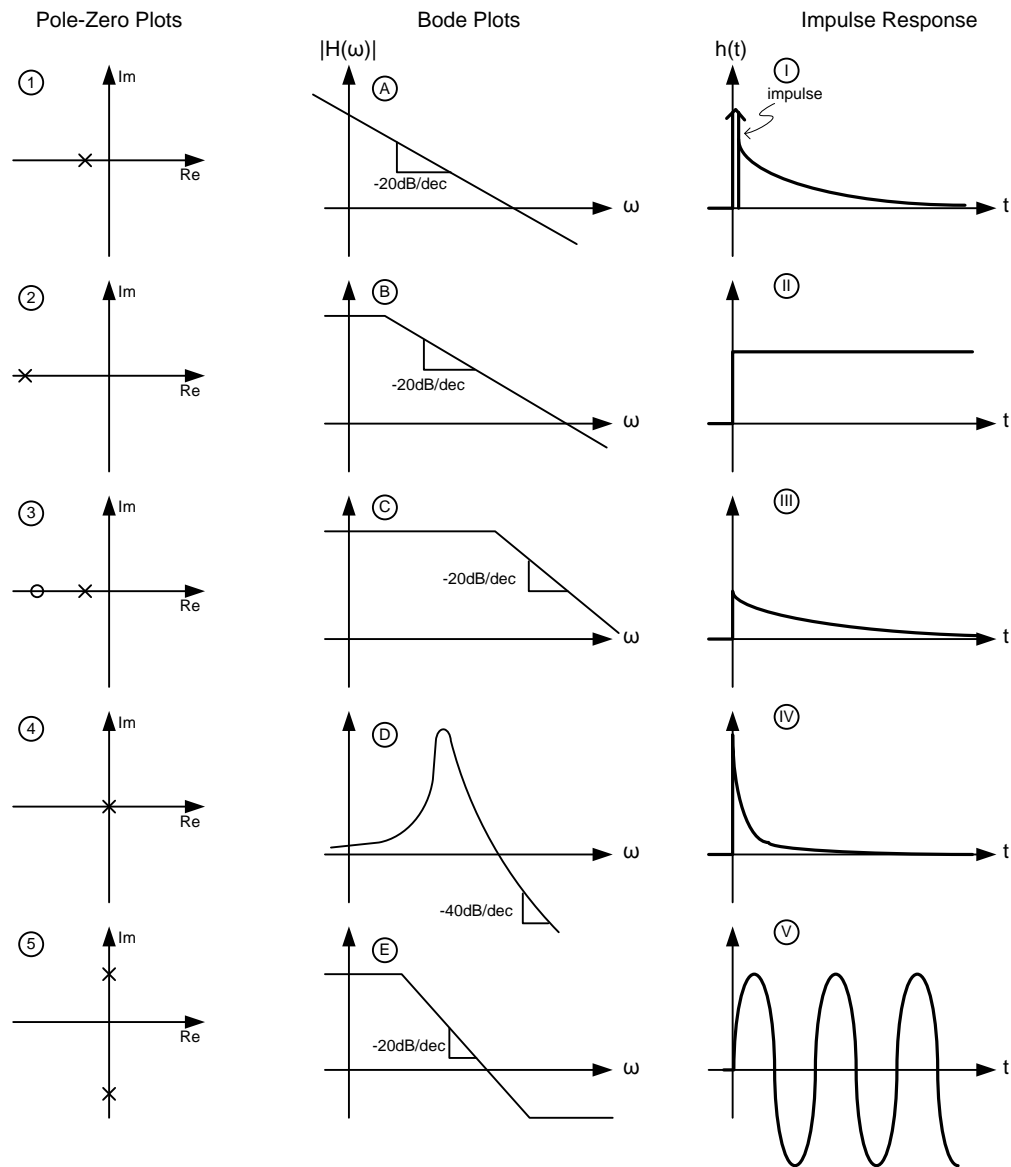



Problem 1

Match each pole-zero plot with a Bode plot, and a time-domain plot of $h(t)$. Hint: try recreating $H(s)$ given the pole-zero plot.



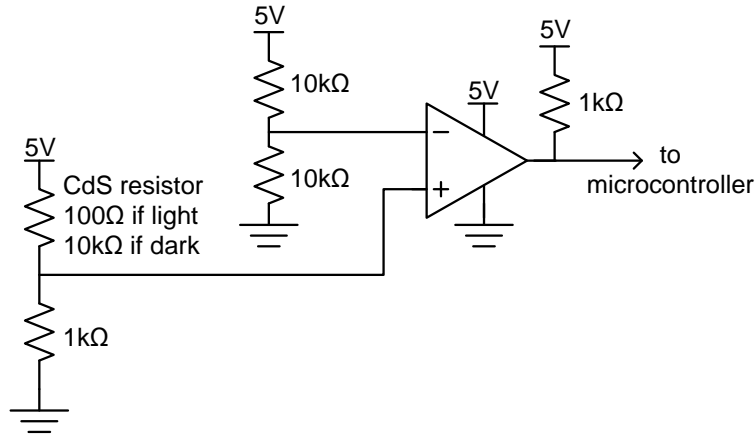Problem 2

You are designing a sensor system for an automatically-closing microprocessor-controlled miniblind system. The light sensor outputs a digital signal to a microprocessor. You design the following circuit:




It works well when exposed to sunlight and in an office lit by incandescent light, but works unreliably in an office lit by fluorescent lights.

- Why?
- What kind of filter (LP, BP, BS, HP) would prevent this?
- Where would you put the filter? What order would you use?
- What would you design its cutoff frequency to be?
- Why would 10kHz be a poor choice for filter cutoff frequency?
- Why would 100μHz be a poor choice for filter cutoff frequency?

Problem 3

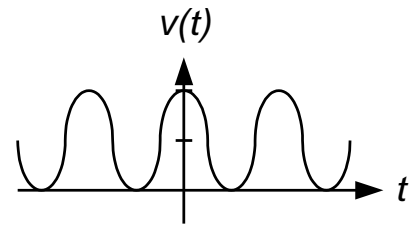
- b) Find numeric values for the Fourier Series coefficients a_0 , a_1 , a_2 , b_1 , and b_2 for $v(t) = 1 + \cos(2t)$ as shown:



- b) If the waveform was very slightly shifted to the right, which components would increase, decrease, or stay the same?

Problem 4

Find c_{-2} , c_{-1} , c_0 , c_1 , and c_2 in complex polar form for the complex Fourier Series coefficients of the waveform.

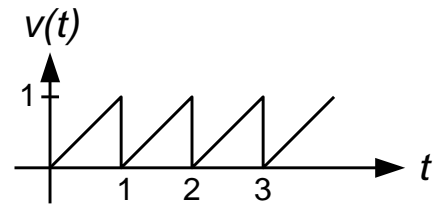

Problem 5

The waveform from Problem 4 is applied to this circuit:
Find the DC and first two harmonics of $v_o(t)$

