

**Given:** The circuit to the right

**Find:**  $i_o(t)$  if  $i_s(t) = 10\sin(2t)\text{A}$  using Fourier Transforms

**Hint:** Use integral formula to find inverse.

Tricky; use sifting property and Euler's Identity

