

**P1 Concept:** Fourier Transforms to solve circuits

**Find:**  $V(\omega)$

Write as a simple ratio of polynomials  
(ie num and den are both polynomials)

**Hints:**

- $s = j\omega$  can simplify algebra, but remember to go back to  $j\omega$  at the end
- if the numerator and denominator are not simple polynomials, -1 on grade
- the numerator has a  $9j\omega$  term

