
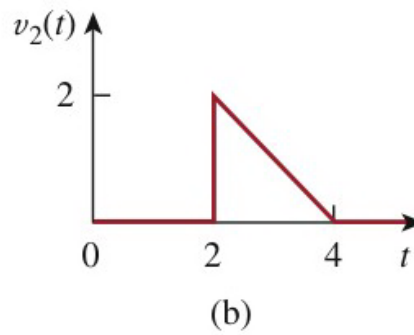


**P1** Sketch the following equations

a.  $u(t-2) + u(t+2)$ , for  $-3 \leq t \leq 3$

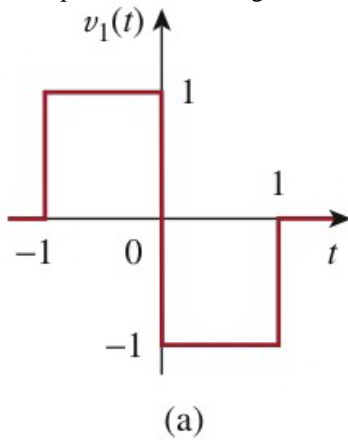b.  $r(t) - r(t-3) + 4u(t-5) - 8u(t-8)$ , for  $-1 \leq t \leq 9$

**P2** Express the following as sums of shifted and scaled  $u(t)$  and  $r(t)$



**P3** Find  $v(t)$  for  $t \geq 0$  in the circuit below. Hint: The only numeric numbers are two integers each between 15 and 25.

